

# *Introduction to Computer Architecture*

## Lecture 3: Combinational Logic

Pooyan Jamshidi

Week 2/3: January 18, 23



**Engineering  
and Computing**

UNIVERSITY OF SOUTH CAROLINA

CSC212: Introduction to Computer Architecture | Spring 2024 | <https://pooyanjamshidi.github.io/csce212/>

[Slides are primarily based on those of Onur Mutlu for the Computer Architecture Course at CMU]

# A Note on Hardware vs. Software

---

- This course might seem like it is only “Computer Hardware”
- However, you will be much more capable if you master both hardware and software (and the interface between them)
  - Can develop better software if you understand the hardware
  - Can design better hardware if you understand the software
  - Can design a better computing system if you understand both
- This course covers the HW/SW interface and microarchitecture
  - We will focus on tradeoffs and how they affect software
- Recall the example chips & platforms we surveyed

# ... but, first ...


---

- Let's understand the fundamentals...
- You can change the world only if you understand it well enough...
  - Especially the basics (fundamentals)
  - Past and present dominant paradigms
  - And, their advantages and shortcomings – tradeoffs
  - And, what remains fundamental across generations
  - And, what techniques you can use and develop to solve problems


# Fundamental Concepts
 
# What is A Computer?

- Three key components
- Computation
- Communication
- Storage/memory




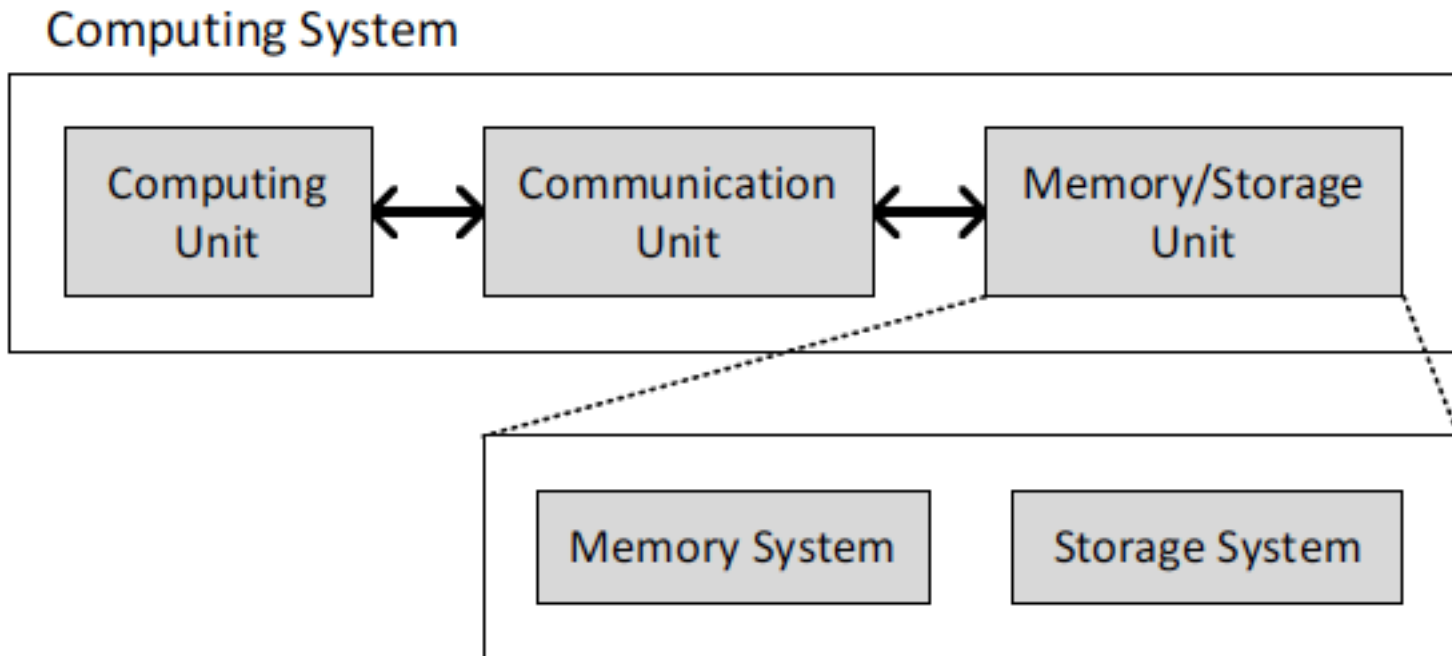Burks, Goldstein, von Neumann, "Preliminary discussion of the logical design of an electronic computing instrument," 1946.



 
# What is A Computer?

- Three key components
- Computation
- Communication
- Storage/memory



Burks, Goldstein, von Neumann, "Preliminary discussion of the logical design of an electronic computing instrument," 1946.


## Computing System

 

# What is A Computer?


---

- We will cover all three components

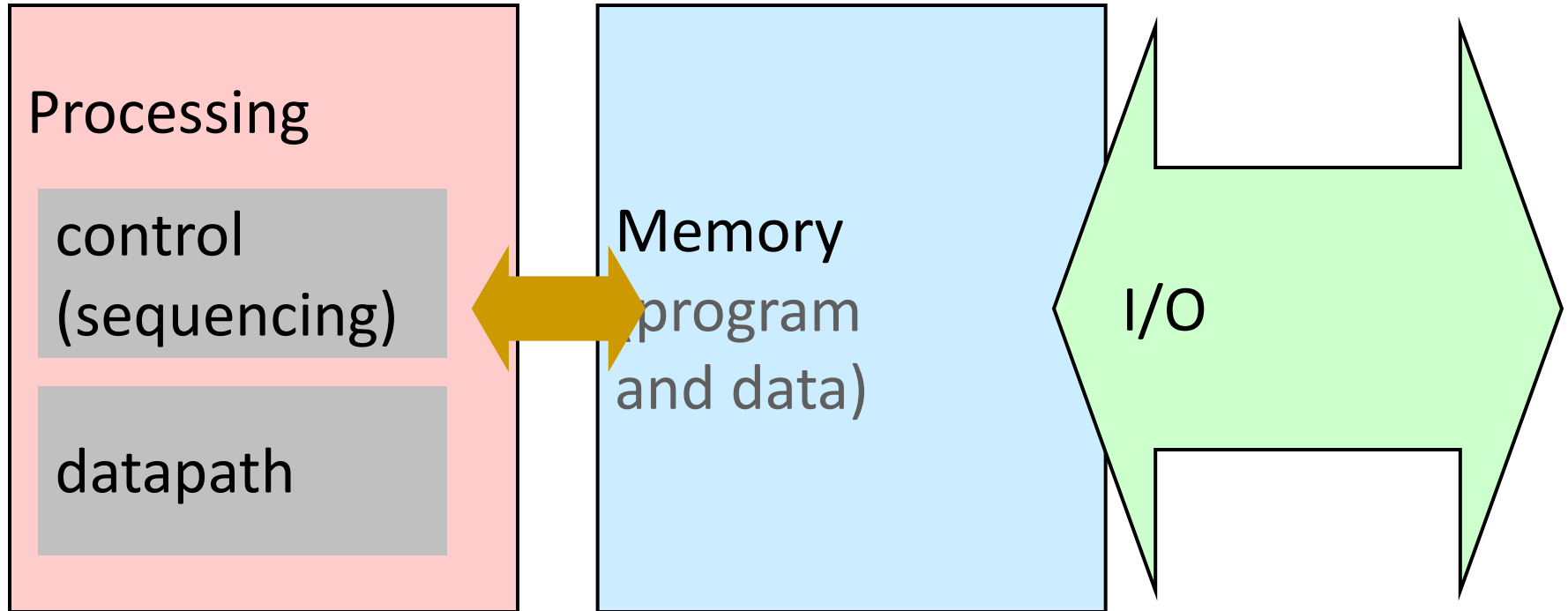

# Recall: The Transformation Hierarchy

---

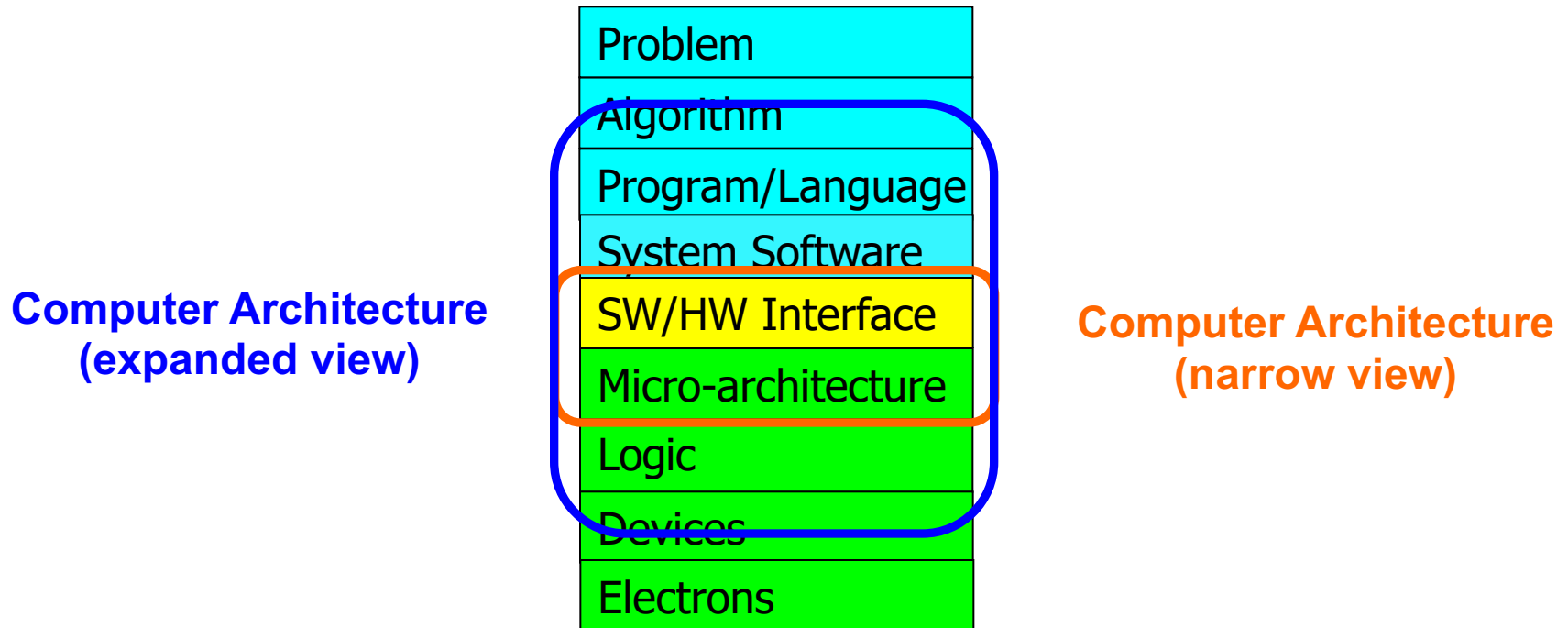



 
# What We Will Cover (I)

---


- Combinational Logic Design
- Hardware Description Languages (Verilog)
- Sequential Logic Design
- Timing and Verification
- ISA (MIPS and LC3b as examples)
- Assembly Programming


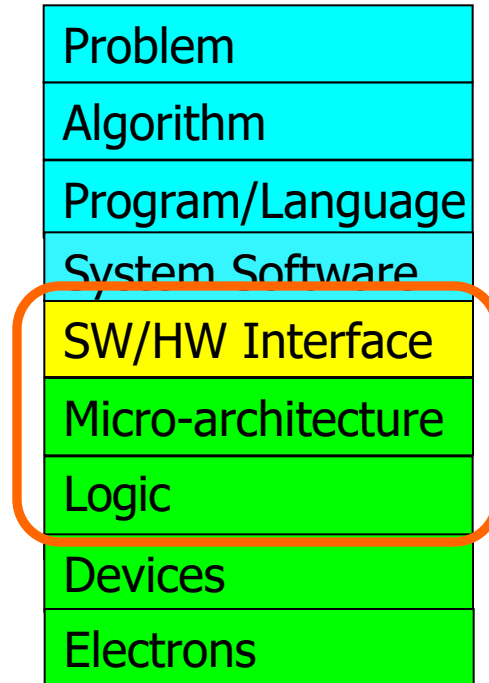
# What We Will Cover (II)

---


- Microarchitecture Fundamentals
- Single-cycle Microarchitectures
- Multi-cycle and Microprogrammed Microarchitectures
- Pipelining
- Issues in Pipelining: Dependence Handling, State Maintenance and Recovery, ...
- Branch Prediction
- Out-of-Order Execution
- Superscalar Execution
- ~~Other Paradigms: Dataflow, VLIW, Systolic, SIMD/GPUs,~~


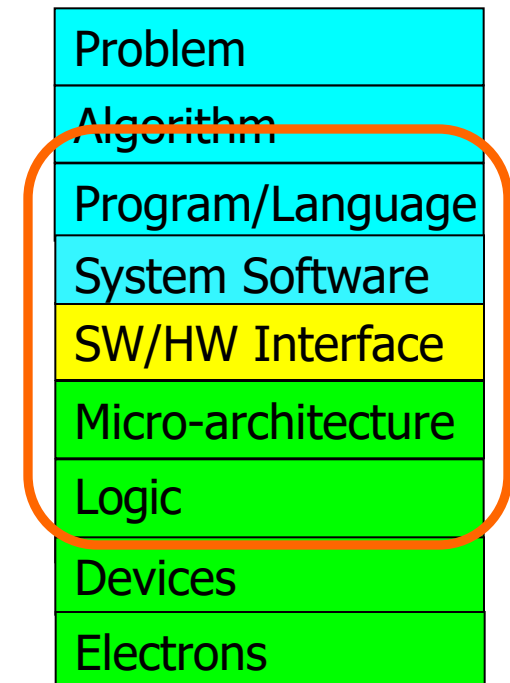
# What We Will NOT Cover (III)

---


- Memory Technology and Organization
- Memory Hierarchy
- Caches
- Multi-Core Caches
- Prefetching
- Virtual Memory


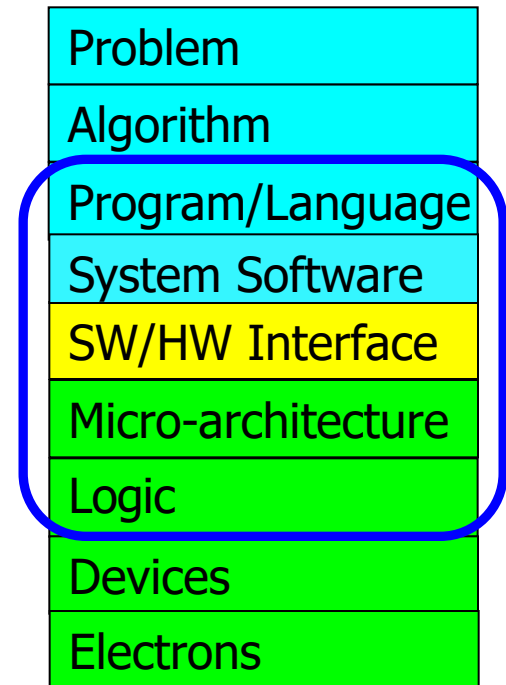
# Processing Paradigms We Will Partially Cover

---

- Pipelining
- Out-of-order execution
- Dataflow (at the ISA level)
- Superscalar Execution
- VLIW
- Decoupled Access-Execute
- Systolic Arrays
- SIMD Processing (Vector & Array)
- GPUs



# Combinational Logic Circuits and Design

# What Will We Learn Today?

---


- Basic building blocks of modern computers
  - Transistors
  - Logic gates
- Boolean algebra
- Combinational logic circuits
- How to use Boolean algebra to represent combinational circuits
- Minimizing logic circuits (if time permits)

# General Purpose vs. Special Purpose Systems

---


## General Purpose

CPU<sub>s</sub>

 


Apple M1

GPU<sub>s</sub>

 

Nvidia GTX 1070


FPGA<sub>s</sub>

 

Xilinx Spartan

## Special Purpose

ASIC<sub>s</sub>

 

Cerebras WSE-2



**Flexible: Can execute any program**

**Easy to program & use**

**Not the best performance & efficiency**

**Efficient & High performance**

**(Usually) Difficult to program & use**

**Inflexible: Limited set of programs**

---

# General Purpose vs. Special Purpose Systems

---

## General Purpose



**Flexible: Can work with any bolt**  
**Easy to use**

**Not the best fit, results or efficiency**

## Special Purpose




**Efficient & High performance**  
**(Usually) Difficult to use**  
**Inflexible: Only for fitting bolts**



# General-Purpose Microprocessors

---

 


# Modern General-Purpose Microprocessors

## 5-nanometer process


The first personal computer chip built with this cutting-edge technology.
 
## 16 billion transistors

The most we've ever put into a single chip.



# Modern General-Purpose Microprocessors

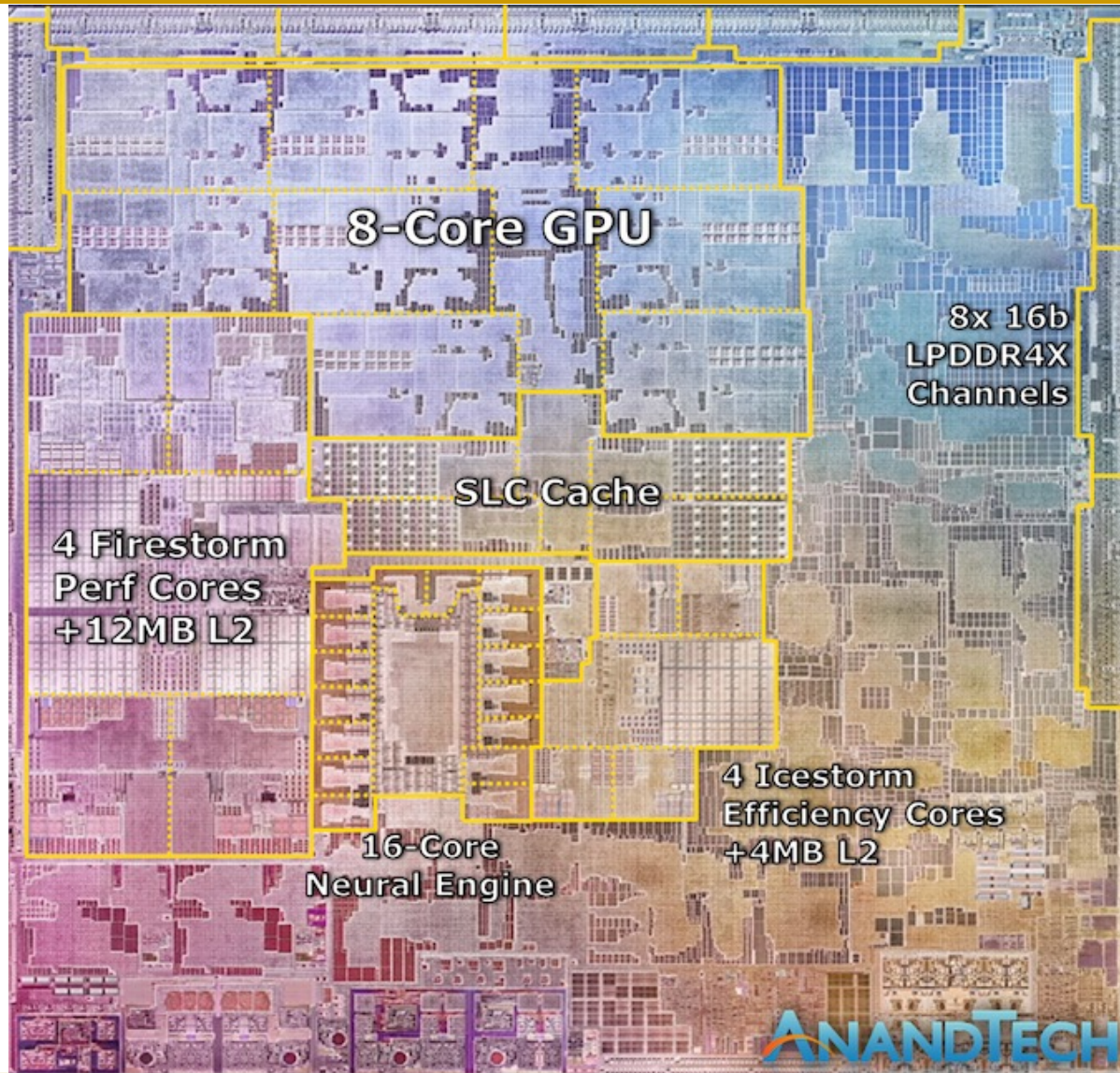


Apple M1,  
2021

# Modern General-Purpose Microprocessors


---



Apple M1

 

Apple M1 Pro

 


Apple M1 Max

# Apple M1 Ultra (2022)


---




Apple M1

 

Apple M1 Pro

 

Apple M1 Max

 

Apple M1 Ultra

# Apple M1 Ultra (2022)

The infographic for the Apple M1 Ultra chip is centered around a dark square containing the Apple logo and the text "M1 ULTRA". Surrounding this central element are several rounded rectangular boxes, each highlighting a specific feature or performance metric. The top row includes ProRes encoding/decoding, Thunderbolt 4 connectivity, a 5 nm process, 114 billion transistors, and a 2.5TB/s interprocessor bandwidth. The middle row features 800GB/s memory bandwidth and a photograph of the chip's silicon interposer. The bottom row lists 20-core CPU, 64-core GPU, 32-core Neural Engine, Secure Enclave, industry-leading performance per watt, and up to 128GB of unified memory.

**ProRes**  
Encode and decode

**Thunderbolt 4**

**5 nm process**

**114 billion Transistors**

**2.5TB/s**  
interprocessor bandwidth

**800GB/s**  
Memory bandwidth

**Apple M1 ULTRA**

**UltraFusion architecture**

**20-core CPU**

**64-core GPU**

**32-core Neural Engine**  
22 trillion operations per second

**Secure Enclave**

**Industry-leading performance per watt**

**Up to 128GB**  
unified memory


# Modern General-Purpose Microprocessors



10nm ESF=Intel 7 Alder Lake die shot (~209mm<sup>2</sup>) from Intel: <https://www.intel.com/content/www/us/en/newsroom/news/12th-gen-core-processors.html>  
Die shot interpretation by Locuza, October 2021


Intel Alder Lake,  
2021

# Modern GPUs

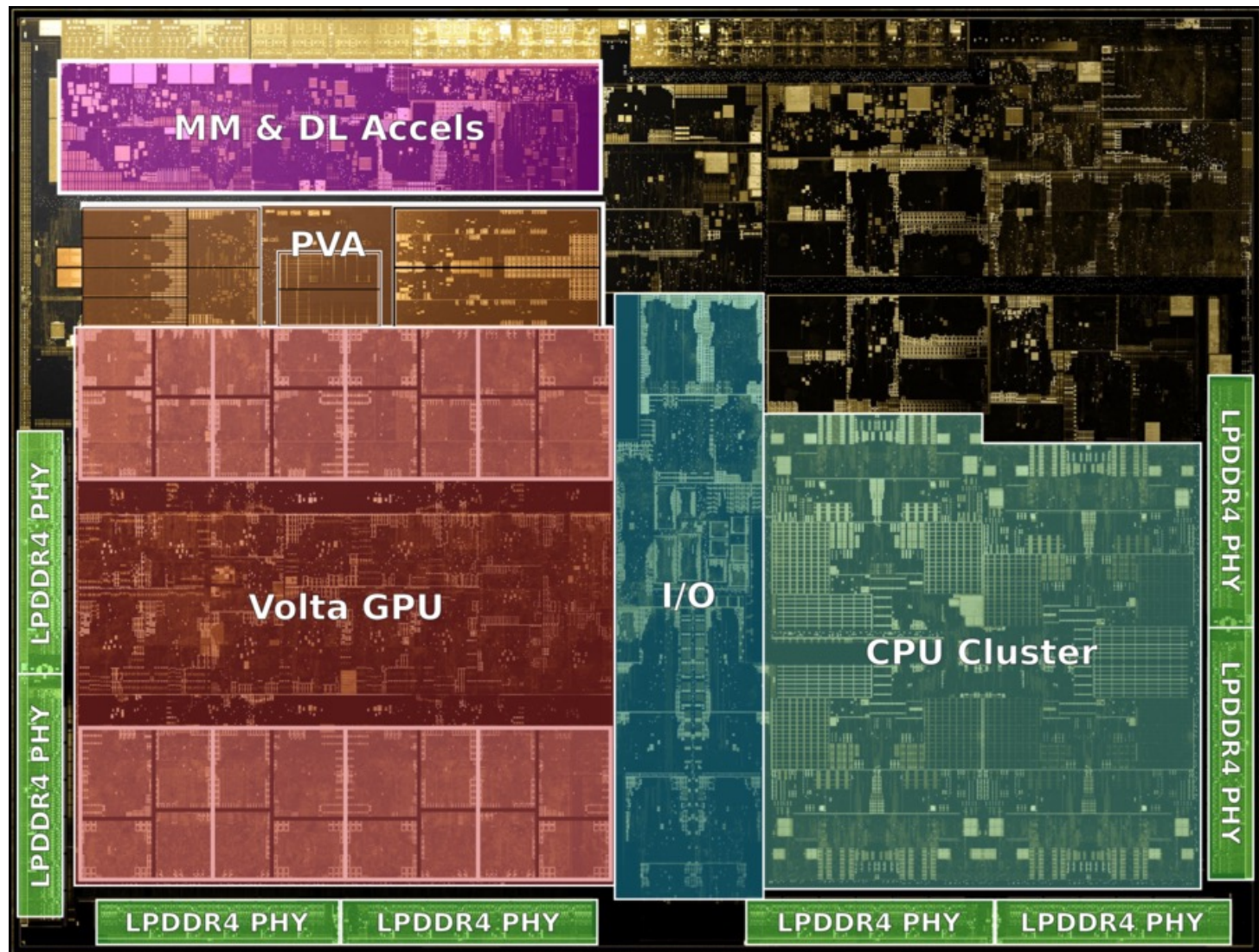




# FPGAs

 


# Modern FPGAs


---

 

 
# Special-Purpose ASICs (App-Specific Integrated Circuits)



# Modern Special-Purpose ASICs

 


**Figure 3.** TPU Printed Circuit Board. It can be inserted in the slot for an SATA disk in a server, but the card uses PCIe Gen3 x16.

 

**Figure 4.** Systolic data flow of the Matrix Multiply Unit. Software has the illusion that each 256B input is read at once, and they instantly update one location of each of 256 accumulator RAMs.

Jouppi et al., “In-Datacenter Performance Analysis of a Tensor Processing Unit”, ISCA 2017.


# Modern Special-Purpose ASICs

 
 
## New ML applications (vs. TPU3):

- Computer vision
- Natural Language Processing (NLP)
- Recommender system
- Reinforcement learning that plays Go


250 TFLOPS per chip in 2021  
vs 90 TFLOPS in TPU3



1 ExaFLOPS per board

<https://spectrum.ieee.org/tech-talk/computing/hardware/heres-how-googles-tpu-v4-ai-chip-stacked-up-in-training-tests>

# Modern Special-Purpose ASICs

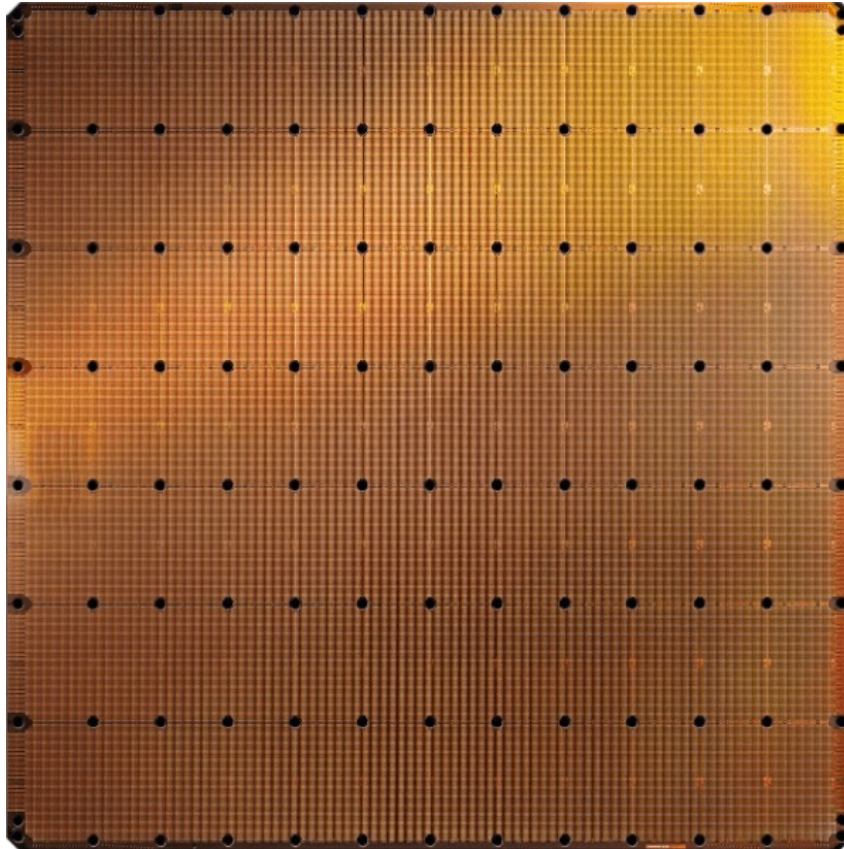

**Cerebras WSE-2**  
2.6 Trillion transistors  
46,225 mm<sup>2</sup>

- The largest ML accelerator chip (2021)
- 850,000 cores




**Largest GPU**  
54.2 Billion transistors  
826 mm<sup>2</sup>  
NVIDIA Ampere GA100

<https://www.anandtech.com/show/14758/hot-chips-31-live-blogs-cerebras-wafer-scale-deep-learning>


<https://www.cerebras.net/cerebras-wafer-scale-engine-why-we-need-big-chips-for-deep-learning/>

# Modern Special-Purpose ASICs
 
## Warehouse-Scale Video Acceleration: Co-design and Deployment in the Wild



**(a) Chip floorplan**

 

**(b) Two chips on a PCBA**

**Figure 5: Pictures of the VCU**

# They All Look the Same


## Microprocessors



## FPGAs



## ASICs

 

**In short:**




Common building block of computers

Reconfigurable hardware, flexible




You customize everything






# They All Look the Same

	Microprocessors	FPGAs	ASICs
			
<b>In short:</b>	Common building block of computers	Reconfigurable hardware, flexible	You customize everything
<b>Program Development Time</b>	minutes	days	months




# They All Look the Same

	Microprocessors	FPGAs	ASICs
			
<b>In short:</b>	Common building block of computers	Reconfigurable hardware, flexible	You customize everything
<b>Program Development Time</b>	minutes	days	months
<b>Performance</b>	0	+	++

# They All Look the Same

	Microprocessors	FPGAs	ASICs
			
<b>In short:</b>	Common building block of computers	Reconfigurable hardware, flexible	You customize everything
<b>Program Development Time</b>	minutes	days	months
<b>Performance</b>	0	+	++
<b>Good for</b>	Ubiquitous Simple to use	Prototyping Small volume	Mass production, Max performance

# They All Look the Same

	Microprocessors	FPGAs	ASICs
			
<b>In short:</b>	Common building block of computers	Reconfigurable hardware, flexible	You customize everything
<b>Program Development Time</b>	minutes	days	months
<b>Performance</b>	0	+	++
<b>Good for</b>	Ubiquitous Simple to use	Prototyping Small volume	Mass production, Max performance
<b>Programming</b>	Executable file	Bit file	Design masks
<b>Languages</b>	C/C++/Java/...	Verilog/VHDL	Verilog/VHDL
<b>Main Companies</b>	Intel, ARM, AMD, Apple, NVIDIA	Xilinx, Altera	TSMC, Globalfoundries

# Labs: Build A Microprocessor on FPGA

Want to learn how these work

## Microprocessors



Common building block of computers

## FPGAs



Reconfigurable hardware, flexible

By programming these

**In short**

**Program Development Time**

**Performance**

**Good for**

**Programming**

**Languages**

**Main Companies**

minutes

0

Ubiquitous  
Simple to use

Executable file

C/C++/Java/...

Intel, ARM, AMD,  
Apple, NVIDIA

days

+

Prototyping

Using this language

**Verilog/VHDL**

Xilinx, Altera

months

++

Mass production.

**Verilog/VHDL**

TSMC,  
Globalfoundries

# All Computers are Built Upon the Same Building Blocks

# Building Blocks of Modern Computers

# Transistors



# Transistors


---

## ■ Computers are built from very large numbers of very small (and relatively simple) structures: **transistors**

- ❑ Intel 4004, in 1971, had **2300** MOS transistors
- ❑ Intel's Pentium IV microprocessor, 2000, was made up of more than **42 Million** MOS transistors
- ❑ Apple's M2 Max, offered for sale in 2022, is made up of more than **67 Billion** MOS transistors
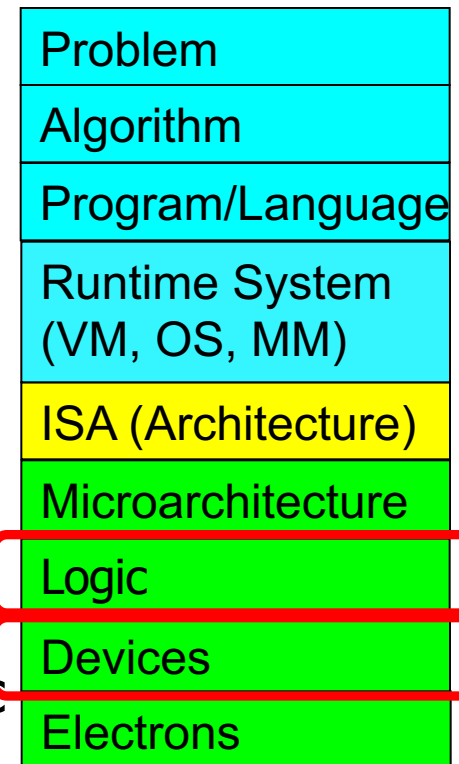
## ■ This lecture


- ❑ How the MOS transistor works (as a logic element)
- ❑ How these transistors are connected to form logic gates
- ❑ How logic gates are interconnected to form larger units that are needed to construct a computer


 
# MOS Transistor

---



- By combining
  - Conductors (**M**etal)
  - Insulators (**O**xide)
  - **S**emiconductors
- We get a Transistor (MOS)
- Why is this useful?
  - We can combine many of these to realize simple logic gates
- The **electrical properties** of metal-oxide semiconductors are well **beyond** the scope of what we want to understand in this course
  - They are below our lowest level of abstraction


  
# Different Types of MOS Transistors

---


- There are two types of MOS transistors: **n-type** and **p-type**



- They both operate “**logically,**” very similar to the way wall switches work

# How Does a Transistor Work?

---

 


- ❑ In order for the lamp to glow, **electrons must flow**
- ❑ In order for electrons to flow, there must be a **closed circuit** from the power supply to the lamp and back to the power supply
- ❑ The lamp can be **turned on and off** by simply manipulating the wall switch to make or break the closed circuit
 
# How Does a Transistor Work?

---

- Instead of the wall switch, we could use an **n-type** or a **p-type** MOS transistor to make or break the closed circuit



Schematic of an **n-type** MOS transistor


If the gate of an **n-type** transistor is supplied with a **high** voltage, the connection from source to drain acts like a **piece of wire** (i.e., the circuit is closed)

Depending on the technology, high voltage can range from 0.3V to 3V


If the gate of the **n-type** transistor is supplied with **zero** voltage, the connection between the source and drain is **broken** (i.e., the circuit is open)
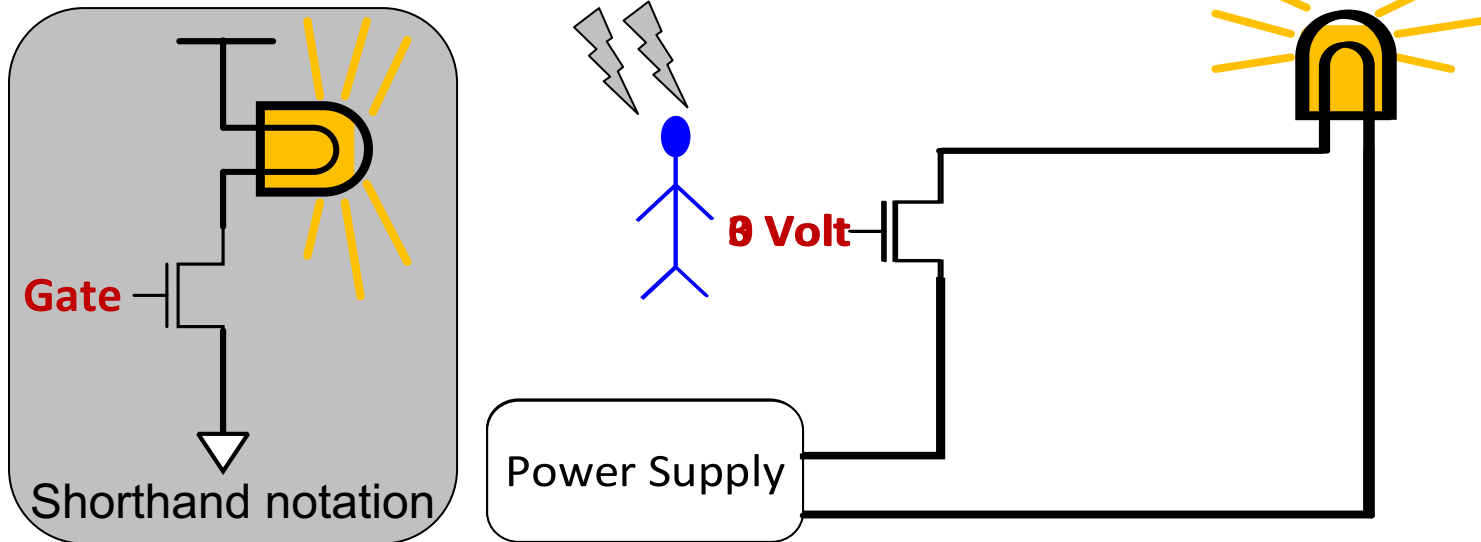
# How Does a Transistor Work?

- The **n-type** transistor in a circuit with a battery and a bulb



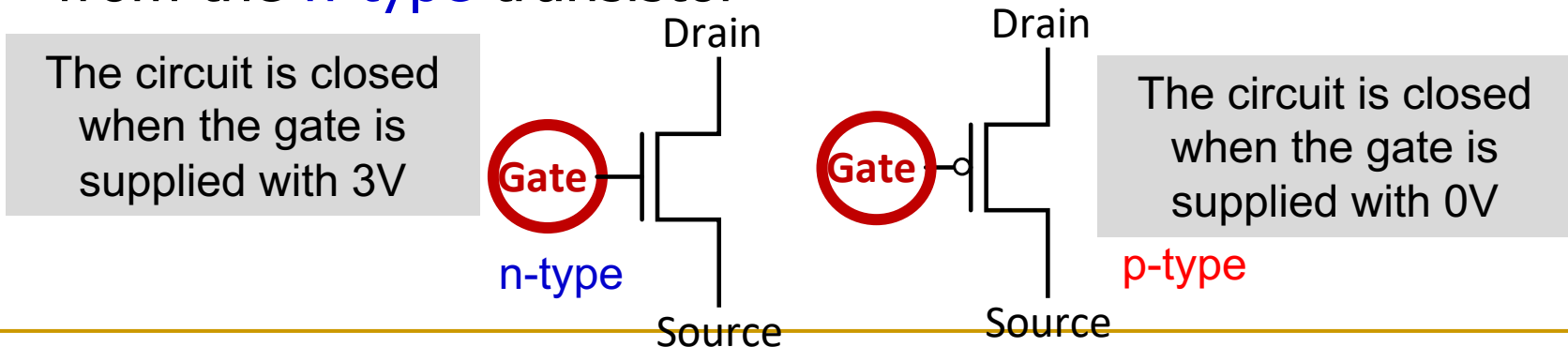- The **p-type** transistor works in exactly the opposite fashion from the **n-type** transistor




# Logic Gates
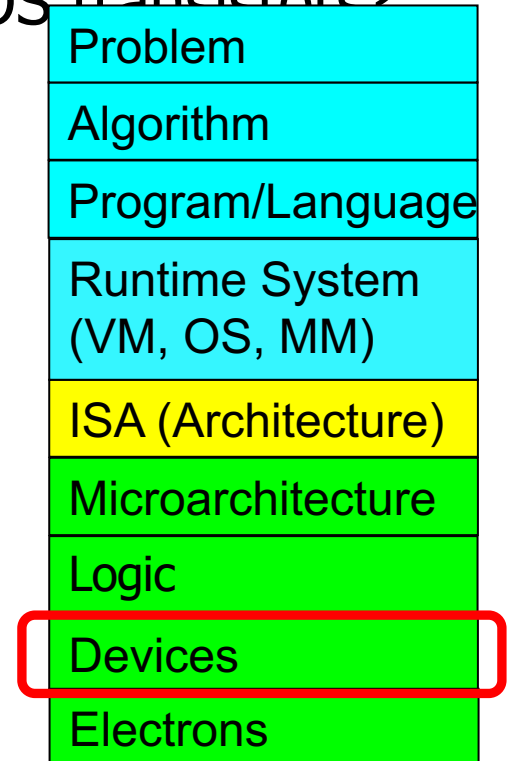
# One Level Higher in the Abstraction

---

- **Now, we know how a MOS transistor works**
- How do we build logic structures out of MOS transistors?
- We construct basic logical units out of individual MOS transistors
- These **logical units** are called **logic gates**
  - They implement simple **Boolean** functions






# Making Logic Blocks Using CMOS Technology

- Modern computers use both **n-type** and **p-type** transistors, i.e. Complementary MOS (CMOS) technology

nMOS + pMOS = CMOS

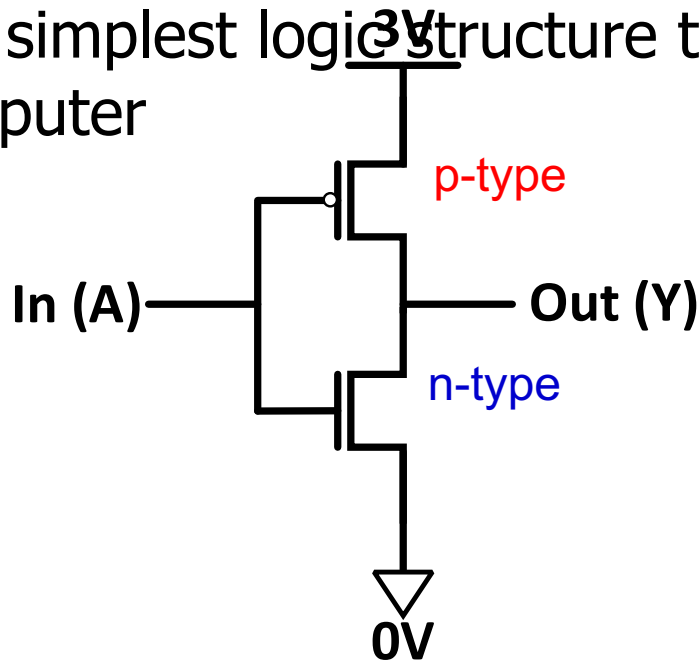
- The simplest logic structure that exists in a modern computer



What does this circuit do?
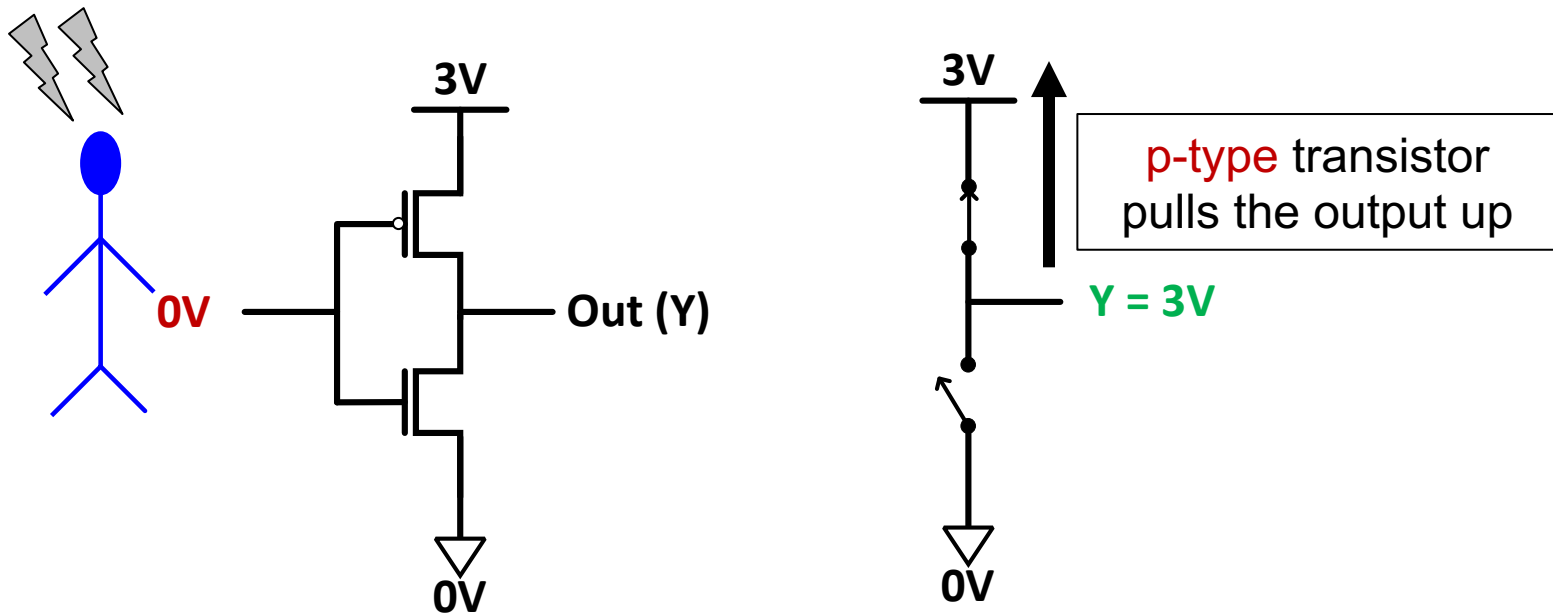
# Functionality of Our CMOS Circuit


What happens when the input is connected to 0V?



**p**-type transistors are good at **pulling up** the voltage
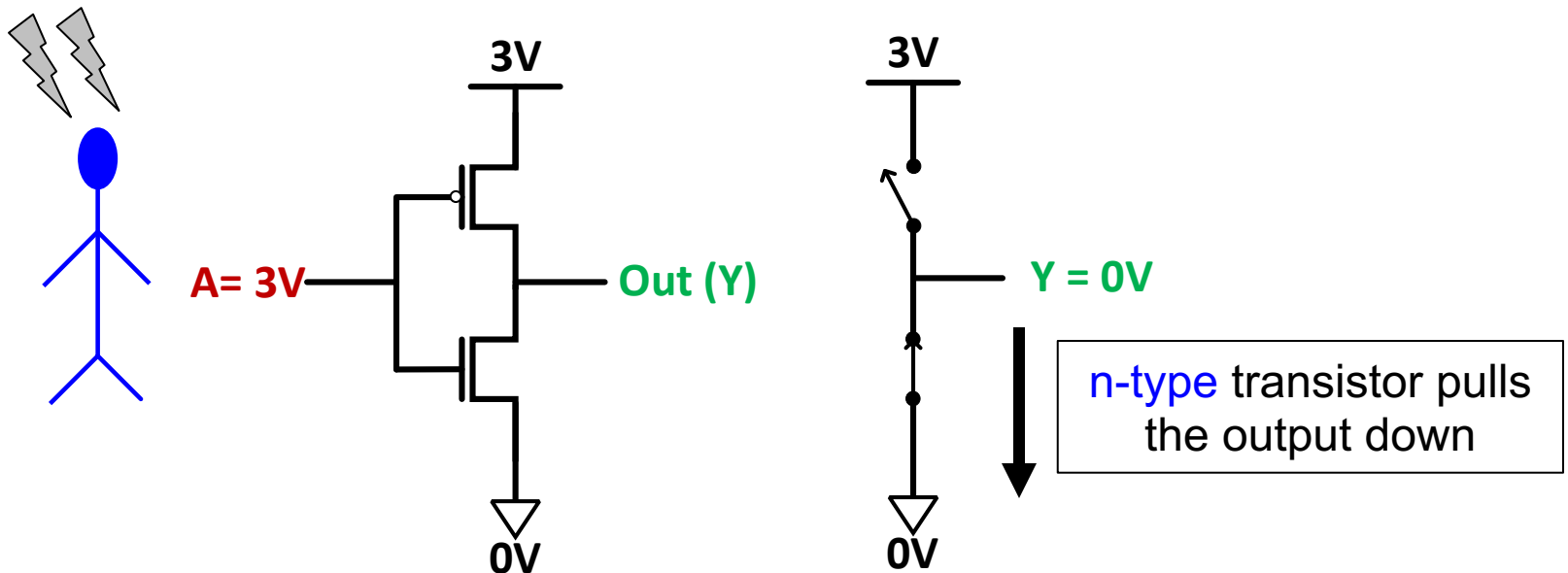
# Functionality of Our CMOS Circuit


What happens when the input is connected to 3V?



n-type transistors are good at pulling down the voltage
 
# CMOS NOT Gate (Inverter)

- This is actually the **CMOS NOT Gate**
- Why do we call it NOT?
  - If  $A = 0V$  then  $Y = 3V$
  - If  $A = 3V$  then  $Y = 0V$
- **Digital circuit:** one possible interpretation
  - Interpret  $0V$  as logical (binary)  $0$  value
  - Interpret  $3V$  as logical (binary)  $1$  value




A	P	N	Y
0	ON	OFF	1
1	OFF	ON	0


$$Y = \bar{A}$$
 
# CMOS NOT Gate (Inverter)

- This is actually the CMOS NOT Gate
- Why do we call it NOT?
  - If  $A = 0V$  then  $Y = 3V$
  - If  $A = 3V$  then  $Y = 0V$
- **Digital circuit:** one possible interpretation
  - Interpret  $0V$  as logical (binary)  $0$  value
  - Interpret  $3V$  as logical (binary)  $1$  value



$$Y = \overline{A}$$

 

We call this a **NOT** gate  
or an **inverter**

(bubble indicates inversion)


**Truth table:** shows what is the logical output of the circuit for each possible input

A	Y
0	1
1	0

# Another CMOS Gate: What Is This?

---


- Let's build more complex gates!

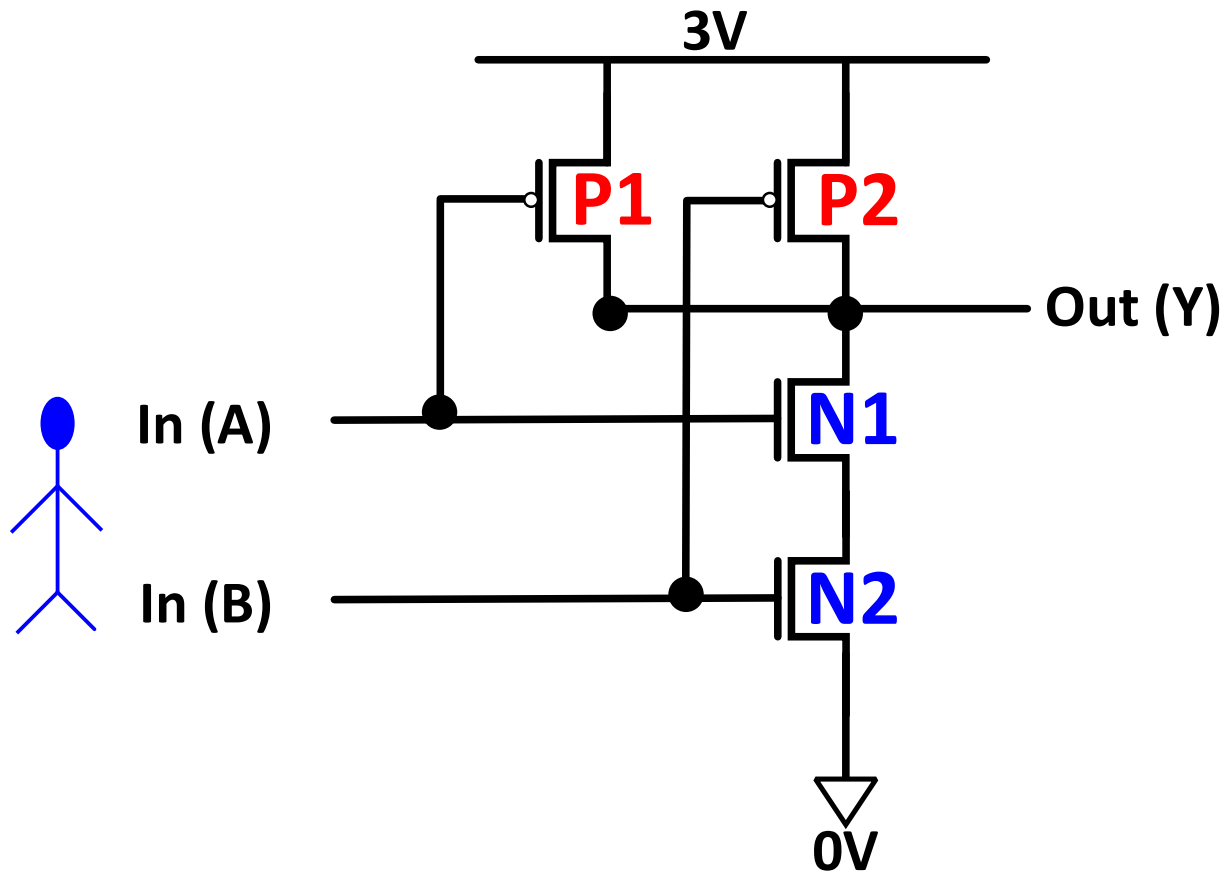
 
# CMOS NAND Gate

- Let's build more complex gates!

$$Y = \overline{A \cdot B} = \overline{AB}$$



A	B	P1	P2	N1	N2	Y
0	0	ON	ON	OFF	OFF	1
0	1	ON	OFF	OFF	ON	1
1	0	OFF	ON	ON	OFF	1
1	1	OFF	OFF	ON	ON	0



- P1 and P2 are in **parallel**; **only one must be ON to pull up the output to 3V**
- N1 and N2 are connected in **series**; **both must be ON to pull down the output to 0V**


  
# CMOS NAND Gate

- Let's build more complex gates!

$$Y = \overline{A \cdot B} = \overline{AB}$$



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

We call this a **NAND** gate  
(bubble indicates inversion)




# CMOS AND Gate


- How can we make an AND gate?

<b>A</b>	<b>B</b>	<b>Y</b>
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = A \cdot B = AB$$

 


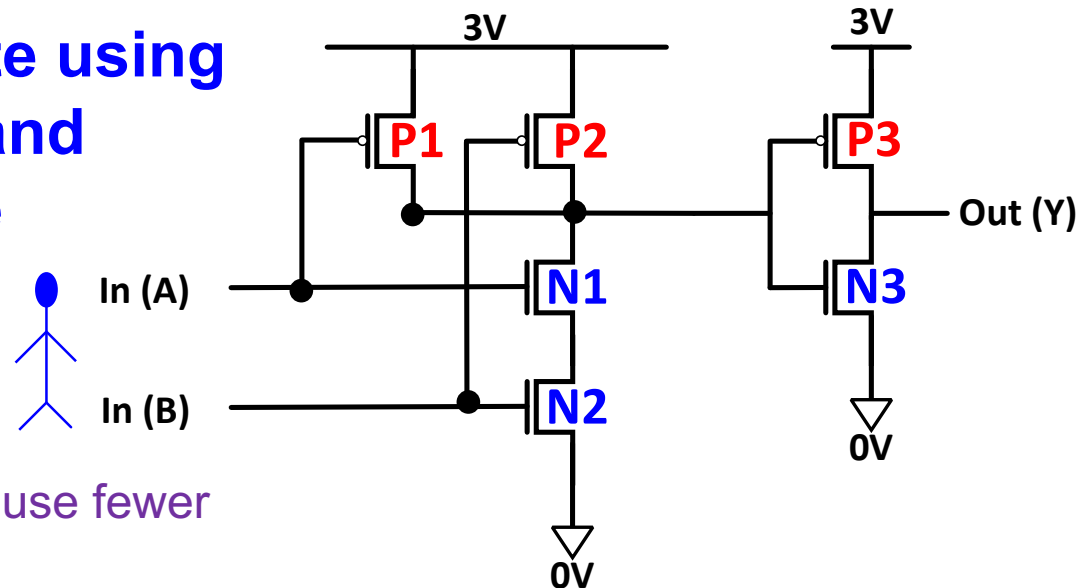We make an **AND** gate using one **NAND** gate and one **NOT** gate




Food for thought: Can we not use fewer transistors for the AND gate?


# CMOS NOT, NAND, AND Gates

 




A	Y
0	1
1	0

 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

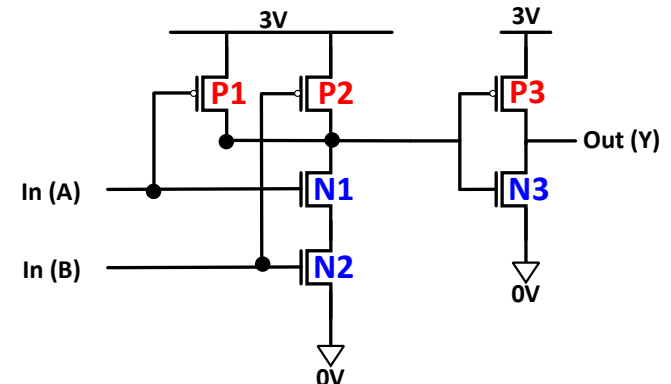  
 
# General CMOS Gate Structure

---

- The general form used to construct any inverting logic gate, such as: NOT, NAND, or NOR
  - The networks may consist of transistors in series or in parallel
  - When transistors are in **parallel**, the network is **ON** if **one** of the transistors is **ON**
  - When transistors are in **series**, the network is **ON** only if **all** transistors are **ON**




**pMOS** transistors are used for pull-up  
**nMOS** transistors are used for pull-down
 
# General CMOS Gate Structure (II)

---



- Exactly one network should be ON, and the other network should be OFF at any given time
  - If both networks are ON at the same time, there is a **short circuit** → likely incorrect operation
  - If both networks are OFF at the same time, the output is **floating** → undefined



**pMOS** transistors are used for pull-up  
**nMOS** transistors are used for pull-down
 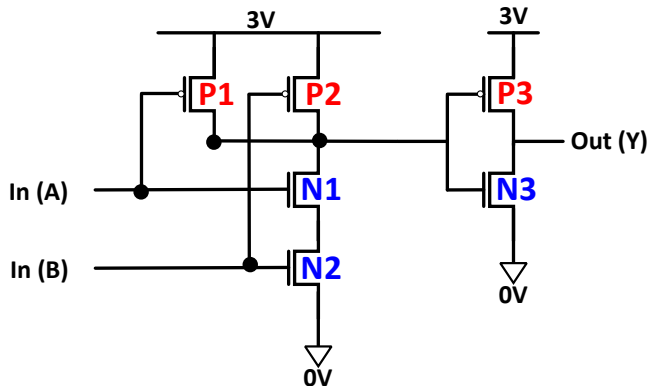
# Digging Deeper: Why This Structure?

- MOS transistors are **imperfect** switches
- pMOS transistors pass 1's well but 0's poorly (holes carry charge)
- nMOS transistors pass 0's well but 1's poorly (electrons carry charge)
- **p**MOS transistors are good at "pulling up" the output
- **n**MOS transistors are good at "pulling down" the output



# Digging Deeper: Latency

- Which one is faster?
  - Transistors in series
  - Transistors in parallel
- Series connections are slower than parallel connections
  - More resistance on the wire
- How do you alleviate this latency?
  - See H&H Section 1.7.8 for an example:  
**pseudo-nMOS Logic**

Used in the past when pMOS transistors could not be fabricated well

 


Figure 1.39 Generic pseudo-nMOS gate

 


Figure 1.40 Pseudo-nMOS four-input NOR gate

# Digging Deeper: Power Consumption

---

- Dynamic Power Consumption
  - Power used to charge capacitance as signals change (0  $\leftrightarrow$  1)
  - $C * V^2 * f$ 
    - C = capacitance of the circuit (wires and gates)
    - V = supply voltage
    - f = charging frequency of the capacitor
- Static Power consumption
  - Power used when signals do not change
  - $V * I_{\text{leakage}}$ 
    - supply voltage \* leakage current
- Energy Consumption
  - Power \* Time

# Common Logic Gates

## Buffer



A	Z
0	0
1	1

## AND



A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

## OR



A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

## XOR



A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

## Inverter



A	Z
0	1
1	0

## NAND



A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

## NOR



A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

## XNOR




A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1



# Larger Gates

---



- We can extend the gates to more than 2 inputs
- Example: 3-input AND gate, 10-input NOR gate
- See your readings

 

**Figure 1.35** Three-input NAND gate schematic

Aside: Moore's Law:  
Enabler of Many Gates on a Chip


# An Enabler: Moore's Law

  

Moore, "Cramming more components onto integrated circuits,"  
Electronics Magazine, 1965.

Component counts double every other year
 
# Microprocessor Transistor Counts 1971-2011 & Moore's Law




Number of transistors on an integrated circuit doubles ~ every two years



# Moore's Law: The number of transistors on microchips doubles every two years

Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important for other aspects of technological progress in computing – such as processing speed or the price of computers.

## Transistor count

 

# Recommended Reading

---

- Moore, “Cramming more components onto integrated circuits,” Electronics Magazine, 1965.
- Only 3 pages
- A quote:  
*"With unit cost falling as the number of components per circuit rises, by 1975 economics may dictate squeezing as many as 65 000 components on a single silicon chip."*
- Another quote:  
*"Will it be possible to remove the heat generated by tens of thousands of components in a single silicon chip?"*


# How Do We Keep Moore's Law: Innovation

---

- **Manufacturing smaller transistors/structures**
  - Some structures are already a few atoms in size
- **Finding materials with better properties**
  - Copper instead of Aluminum (better conductor)
  - Hafnium Oxide, air for Insulators
  - Making sure all materials are compatible is the challenge
- **Enabling precision manufacturing**
  - Extreme ultraviolet (EUV) light to pattern <10nm structures
- **Creating new device technologies**
  - FinFET, Gate All Around transistor, Single Electron Transistor...


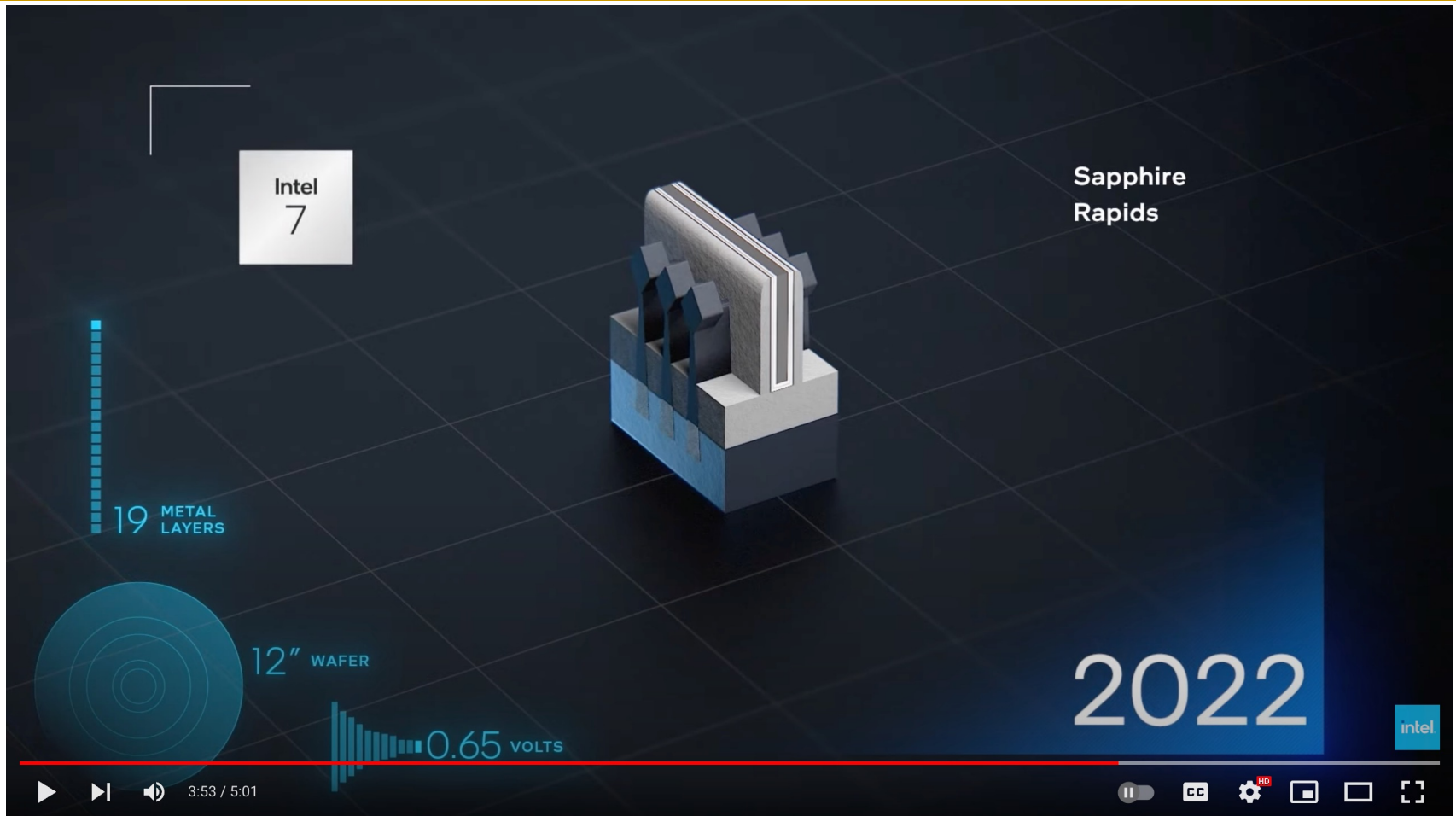
# A 5-Minute Video on Transistor Innovation



Evolution of Transistor Innovation

12,441 views • Feb 22, 2022


628 DISLIKE SHARE CLIP SAVE ...

 Intel Technology  
15.5K subscribers

SUBSCRIBE

<https://www.youtube.com/watch?v=Z7M8etXUEUU>
 
# A 5-Minute Video on Transistor Innovation



## Evolution of Transistor Innovation

12,460 views • Feb 22, 2022


628 DISLIKE SHARE CLIP SAVE ...



SUBSCRIBE

<https://www.youtube.com/watch?v=Z7M8etXUEUU>

# Enabling Manufacturing Tech: EUV

 

#EUV #chip #Intel

Behind this Door: Learn about EUV, Intel's Most Precise, Complex Machine

78,354 views • Dec 21, 2021

LIKE DISLIKE SHARE CLIP SAVE ...


intel Intel Newsroom  
25.9K subscribers

SUBSCRIBE

<https://www.youtube.com/watch?v=Jv40Viz-KTc>

# Innovation At the Bottom Enables Computing

---

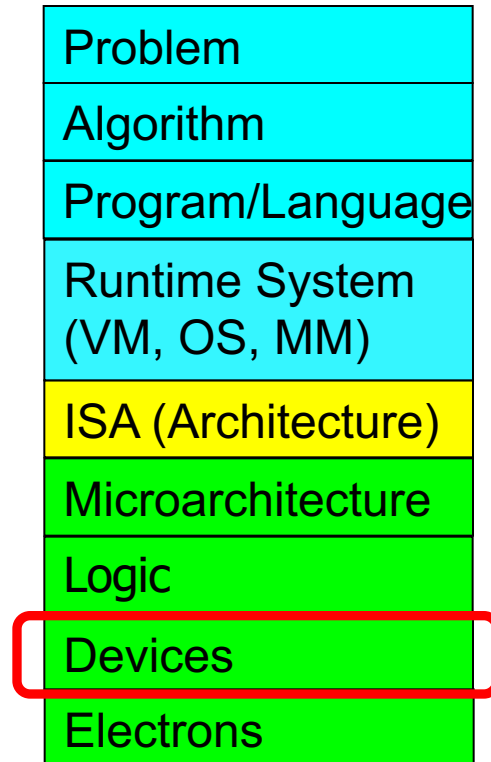

# Historical: Opportunities at the Bottom

---

## There's Plenty of Room at the Bottom

---

From Wikipedia, the free encyclopedia

**"There's Plenty of Room at the Bottom: An Invitation to Enter a New Field of Physics"** was a lecture given by [physicist Richard Feynman](#) at the annual [American Physical Society](#) meeting at [Caltech](#) on December 29, 1959.<sup>[1]</sup> Feynman considered the possibility of direct manipulation of individual atoms as a more powerful form of synthetic chemistry than those used at the time. Although versions of the talk were reprinted in a few popular magazines, it went largely unnoticed and did not inspire the conceptual beginnings of the field. Beginning in the 1980s, nanotechnology advocates cited it to establish the scientific credibility of their work.

# Historical: Opportunities at the Bottom (II)

---

## There's Plenty of Room at the Bottom

---

From Wikipedia, the free encyclopedia

Feynman considered some ramifications of a general ability to manipulate matter on an atomic scale. He was particularly interested in the possibilities of denser computer circuitry, and microscopes that could see things much smaller than is possible with scanning electron microscopes. These ideas were later realized by the use of the scanning tunneling microscope, the atomic force microscope and other examples of scanning probe microscopy and storage systems such as Millipede, created by researchers at IBM.

Feynman also suggested that it should be possible, in principle, to make nanoscale machines that "arrange the atoms the way we want", and do chemical synthesis by mechanical manipulation.

He also presented the possibility of "swallowing the doctor", an idea that he credited in the essay to his friend and graduate student Albert Hibbs. This concept involved building a tiny, swallowable surgical robot.

# Extra Assignment 2: Moore's Law (I)

---

- **Paper review**
- G.E. Moore. "Cramming more components onto integrated circuits," Electronics magazine, 1965
  
- **Optional Assignment – for 1% extra credit**
  - **Write a 1-page review**
  - Upload PDF file to Gradescope – Deadline: March 1

# How to Do the Paper/Talk Reviews

---

- 1: **Summary**
  - What is the problem the paper is trying to solve?
  - What are the key ideas of the paper? Key insights?
  - What are the key mechanisms? What is the implementation?
  - What are the key results? Key conclusions?
- 2: **Strengths** (most important ones)
  - Does the paper solve the problem well? Is it well written? ...
- 3: **Weaknesses** (most important ones)
  - This is where you should **think critically**. Every paper/idea has a weakness. This does not mean the paper is necessarily bad. It means there is room for improvement and future research can accomplish this.
- 4: Can you do (much) better? Present your **thoughts/ideas**.
- 5: **Takeaways**: What you learned/enjoyed/disliked? Why?
- 6: Any **other comments** you would like to make.
- **Review should be short and concise (~one page)**



# Advice on Paper/Talk Reviews

---

- When doing the reviews, be very critical
- Always think about better ways of solving the problem or related problems
  - Question the problem as well
- This is how things progress in science and engineering (or anywhere), and how you can make big leaps
  - By critical analysis
- Sample reviews provided online

# Extra Assignment 2: Moore's Law (II)

---

- Example reviews on “Main Memory Scaling: Challenges and Solution Directions” ([link to the paper](#))
  - [Review 1](#)
  - [Review 2](#)
- Example review on “Staged memory scheduling: Achieving high performance and scalability in heterogeneous systems” ([link to the paper](#))
  - [Review 1](#)

# Combinational Logic Circuits



# We Can Now Build Logic Circuits

---


Now, we understand the workings of the basic logic gates

What is our next step?

Build some of the logic structures that are important components of the microarchitecture of a computer

- A logic circuit is composed of:


- Inputs
- Outputs

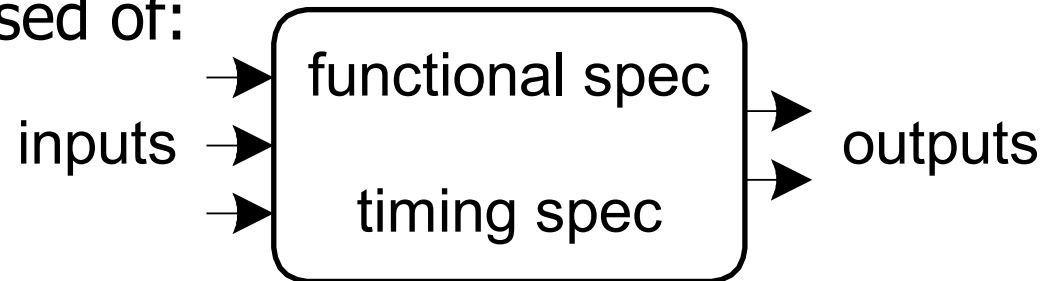

- *Functional specification* (describes relationship between inputs and outputs)
- *Timing specification* (describes the delay between inputs changing and outputs responding)

# Types of Logic Circuits

---

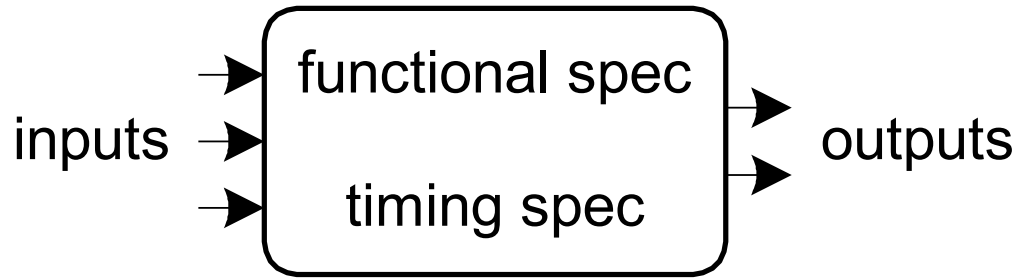

## ■ **Combinational Logic**

- ❑ Memoryless
- ❑ Outputs are strictly dependent on the combination of input values that are being applied to circuit *right now*
- ❑ In some books called Combinatorial Logic

## ■ **Later we will learn: Sequential Logic**

- ❑ Has memory
  - Structure stores history → Can "store" data values
- ❑ Outputs are determined by previous (historical) and current values of inputs

# Boolean Logic Equations




# Functional Specification

---

- **Functional specification** of outputs in terms of inputs
- What do we mean by “function”?
  - Unique **mapping** from input values to output values
  - The **same** input values produce the **same** output value every time
  - **No memory** (does not depend on the history of input values)
- **Example (full 1-bit adder – more later):**

$$S = F(A, B, C_{in})$$

$$C_{out} = G(A, B, C_{in})$$

 

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$



# Simple Equations: NOT / AND / OR

$\bar{A}$  (reads "not A") is 1 iff A is 0



A	$\bar{A}$
0	1
1	0

$A \cdot B$  (reads "A and B") is 1 iff A and B are both 1



A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

$A + B$  (reads "A or B") is 1 iff either A or B is 1




A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1




 
# Boolean Algebra: Big Picture

- An algebra on 1's and 0's
  - with AND, OR, NOT operations
- What you start with
  - **Axioms:** basic things about objects and operations you just assume to be true at the start
- What you derive first
  - **Laws and theorems:** allow you to manipulate Boolean expressions
  - ...also allow us to do **simplification on Boolean expressions**
- What you derive later
  - More "sophisticated" properties useful for manipulating digital designs represented in the form of Boolean equations



# Boolean Algebra: Axioms

## *Formal version*

1.  $B$  contains at least two elements,  
 $0$  and  $1$ , such that  $0 \neq 1$

2. *Closure*  $a, b \in B$ ,  
(i)  $a + b \in B$   
(ii)  $a \cdot b \in B$

3. *Commutative Laws*:  $a, b \in B$ ,  
(i)  
(ii)

4. *Identities*:  $0, 1 \in B$   
(i)  
(ii)

5. *Distributive Laws*:  
(i)  
(ii)

6. *Complement*:  
(i)  
(ii)

## *English version*

Math formality...

Result of AND, OR stays  
in set you start with

For primitive AND, OR of  
2 inputs, order doesn't matter

There are identity elements  
for AND, OR, that give you back  
what you started with

- distributes over  $+$ , just like algebra  
...but  $+$  distributes over  $\cdot$ , also (!!)

There is a complement element;  
AND/ORing with it gives the identity elem.



# Boolean Algebra: Duality

---

## ■ Observation

- All the axioms come in “dual” form
- Anything true for an expression also true for its dual
- So any derivation you could make that is true, can be flipped into dual form, and it stays true

## ■ Duality — More formally

- A dual of a Boolean expression is derived by replacing
  - Every **AND** operation with... an **OR** operation
  - Every **OR** operation with... an **AND**
  - Every **constant 1** with... a **constant 0**
  - Every **constant 0** with... a **constant 1**

**Example**

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$
$$\rightarrow a + (b \cdot c) = (a + b) \cdot (a + c)$$



# Boolean Algebra: Useful Laws

---

Dual



*Operations with 0 and 1:*

1.  $X + 0 = X$

2.  $X + 1 = 1$

1D.  $X \cdot 1 = X$

2D.  $X \cdot 0 = 0$

AND, OR with identities gives you back the original variable or the identity

---

*Idempotent Law:*

3.  $X + X = X$

3D.  $X \cdot X = X$

AND, OR with self = self

---

*Involution Law:*

4.  $\overline{\overline{X}} = X$

double complement = no complement

---

*Laws of Complementarity:*

5.  $X + \overline{X} = 1$

5D.  $X \cdot \overline{X} = 0$

AND, OR with complement gives you an identity

---

*Commutative Law:*

6.  $X + Y = Y + X$

6D.  $X \cdot Y = Y \cdot X$

Just an axiom...



# Useful Laws (continued)

---

## *Associative Laws:*

$$7. (X + Y) + Z = X + (Y + Z) \\ = X + Y + Z$$

$$7D. (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z) \\ = X \cdot Y \cdot Z$$

Parenthesis order  
does not matter

## *Distributive Laws:*

$$8. X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$8D. X + (Y \cdot Z) = (X + Y) \cdot (X + Z) \quad \text{Axiom}$$

## *Simplification Theorems:*

9.

9D.

10.

10D.

11.

11D.

Useful for  
simplifying  
expressions

Actually worth remembering — they show up a lot in real designs...



# Boolean Algebra: Proving Things

---

*Proving theorems via axioms of Boolean Algebra:*

**EX: Prove the theorem:  $X \cdot Y + X \cdot \bar{Y} = X$**

**Distributive (5)**

**Complement (6)**

**Identity (4)**

**EX2: Prove the theorem:  $X + X \cdot Y = X$**

**Identity (4)**

**Distributive (5)**

**Identity (2)**

**Identity (4)**



# DeMorgan's Law: Enabling Transformations

---

*DeMorgan's Law:*

$$12. \overline{(X + Y + Z + \dots)} = \bar{X} \cdot \bar{Y} \cdot \bar{Z} \cdot \dots$$

$$12D. \overline{(X \cdot Y \cdot Z \cdot \dots)} = \bar{X} + \bar{Y} + \bar{Z} + \dots$$

---

## ■ Think of this as a transformation

- Let's say we have:

$$F = A + B + C$$

- Applying DeMorgan's Law (12), gives us

$$F = \overline{\overline{(A + B + C)}} = \overline{(\bar{A} \cdot \bar{B} \cdot \bar{C})}$$

At least one of A, B, C is TRUE --> It is **not** the case that A, B, C are **all** false

---

# DeMorgan's Law (Continued)

These are conversions between **different types of logic functions**  
They can prove useful **if you do not have every type of gate...**  
**Or, if some types of gates are more desirable to use than others...**

$$A = \overline{(X + Y)} = \bar{X}\bar{Y}$$


**NOR is equivalent to AND  
with inputs complemented**



X	Y	$\overline{X+Y}$	$\bar{X}$	$\bar{Y}$	$\bar{X}\bar{Y}$
0	0	1	1	1	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	0

$$B = \overline{(XY)} = \bar{X} + \bar{Y}$$

 **NAND is equivalent to OR  
with inputs complemented**



X	Y	$\overline{XY}$	$\bar{X}$	$\bar{Y}$	$\bar{X} + \bar{Y}$
0	0	1	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0





# Using Boolean Equations to Represent a Logic Circuit



# Boolean Equations Enable Us To...

---

- Represent the function of a combinational logic block
  - Functional Specification
- Methodically transform the function into simpler functions
  - which lead to different hardware realizations
  - Logic Minimization or Logic Simplification
  - We can automate this process → Computer-Aided Design or Electronic Design Automation
- Different Boolean expressions lead to different logic gate implementations
  - Different hardware area, cost, latency, energy properties



# Standardized Function Representations

---

- Enable a single, universally-agreed-on way of representing a Boolean function starting from its truth table
  - Also called “canonical representations”
  
- Sum of Products (SOP) form
  
- Product of Sums (POS) form

# Sum of Products Form: Key Idea

---

- Assume **we have the truth table of Boolean Function F**
- How do we express the function in terms of the inputs in a **standard** manner?
- Idea: **Sum of Products** form
- **Express the truth table as a two-level Boolean expression**
  - that contains **all** input variable combinations that result in a 1 output
  - If ANY of the combinations of input variables that results in a 1 is TRUE, then the output is 1
  - **$F = \text{OR of all input variable combinations that result in a 1}$**

# Some Definitions (for a 3-Input Function)

---

- **Complement:** variable with a bar over it  
 $\bar{A}, \bar{B}, \bar{C}$
- **Literal:** variable or its complement  
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- **Implicant:** product (AND) of literals  
 $(A \cdot B \cdot \bar{C}), (\bar{A} \cdot C), (B \cdot \bar{C})$
- **Minterm:** product (AND) that includes **all** input variables  
 $(A \cdot B \cdot \bar{C}), (\bar{A} \cdot \bar{B} \cdot C), (\bar{A} \cdot B \cdot \bar{C})$
- **Maxterm:** sum (OR) that includes **all** input variables  
 $(A + \bar{B} + \bar{C}), (\bar{A} + B + \bar{C}), (A + B + \bar{C})$

# Two-Level Canonical (Standard) Forms

---

- **Truth table** is the unique **signature** of a Boolean *function* ...
  - But, it is an expensive representation
- A Boolean function can have many alternative Boolean expressions
  - i.e., many alternative Boolean expressions (and gate realizations) may have the same truth table (and function)
  - **If they all specify the same thing, why do we care?**
    - Different Boolean expressions lead to different logic gate implementations → Different cost, latency, energy properties
- **Canonical form: standard form for a Boolean expression**
  - Provides a unique algebraic signature

# Two-Level Canonical Forms: SOP

## Sum of Products Form (SOP)

Also known as **disjunctive normal form** or **minterm expansion**

A	B	C	F	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$\bar{A}BC$
1	0	0	1	$A\bar{B}\bar{C}$
1	0	1	1	$A\bar{B}C$
1	1	0	1	$AB\bar{C}$
1	1	1	1	$ABC$


$F = \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$

- Each row in a truth table has a minterm
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)

All Boolean equations can be written in SOP form

Find all the input combinations (minterms) for which the output of the function is TRUE.

# SOP Form — Why Does It Work?

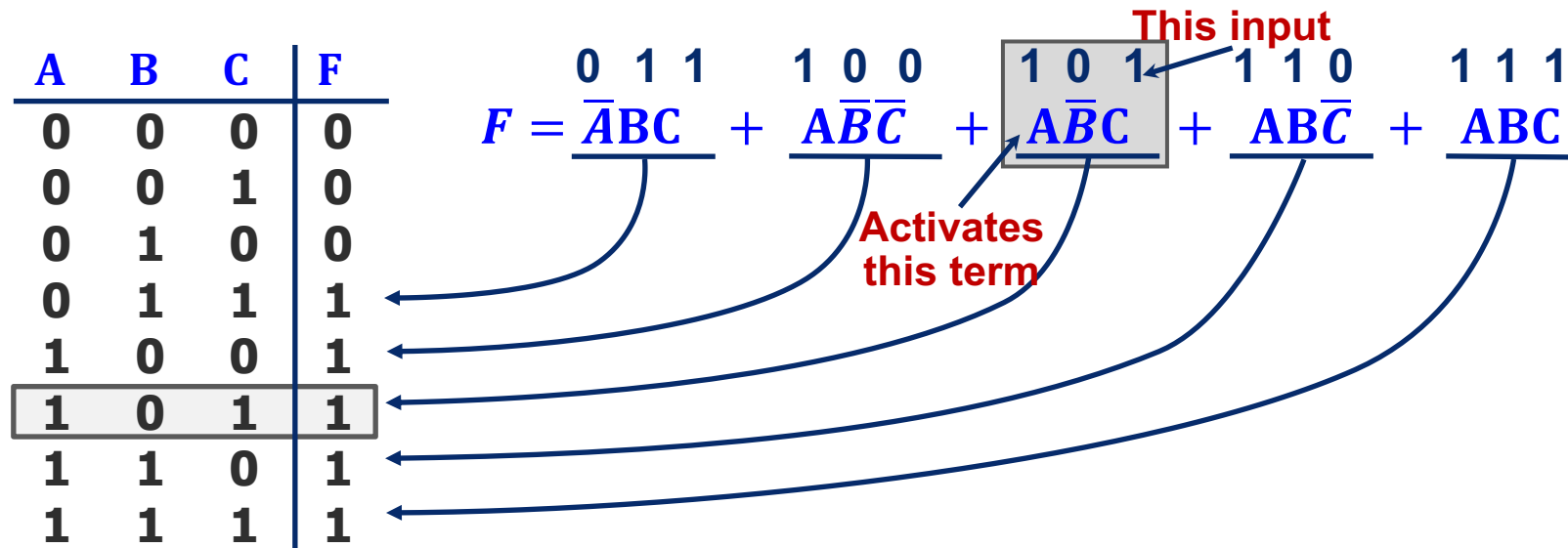

- Only the shaded product term —  $\overline{A}\overline{B}C = 1 \cdot 0 \cdot 1$  — will be 1
- No other product terms will “turn on” — they will all be 0
- So if inputs A B C correspond to a product term in expression,
  - We get  $0 + 0 + \dots + 1 + \dots + 0 + 0 = 1$  for output
- If inputs A B C do not correspond to any product term in expression
  - We get  $0 + 0 + \dots + 0 = 0$  for output

The function evaluates to TRUE (i.e., output is 1)  
 if **any** of the **Products** (minterms) causes the output to be 1



# Standard Notation for SOP Form

- Standard “shorthand” notation
  - If we agree on the **order** of the variables in the rows of truth table...
    - then we can enumerate each row with the decimal number that corresponds to the binary number created by the input pattern

A	B	C	F	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	
1	0	0	1	<b>100 = decimal 4 so this is minterm #4, or m4</b>
1	0	1	1	
1	1	0	1	
1	1	1	1	<b>111 = decimal 7 so this is minterm #7, or m7</b>

f =


**We can write this as a sum of products**

Or, we can use a summation notation

# Canonical SOP Form

A	B	C	minterms
0	0	0	$\overline{A}\overline{B}\overline{C} = m_0$
0	0	1	$\overline{A}\overline{B}C = m_1$
0	1	0	$\overline{A}B\overline{C} = m_2$
0	1	1	$\overline{A}BC = m_3$
1	0	0	$A\overline{B}\overline{C} = m_4$
1	0	1	$A\overline{B}C = m_5$
1	1	0	$AB\overline{C} = m_6$
1	1	1	$ABC = m_7$

 Shorthand Notation for Minterms of 3 Variables



2-Level AND/OR Realization

*F in canonical form:*

$$F(A,B,C) = \sum m(3,4,5,6,7) \\ = m_3 + m_4 + m_5 + m_6 + m_7$$

*F =*


*canonical form  $\neq$  minimal form*

*F*

# From SOP to Gates

- **SOP (sum-of-products) leads to two-level logic**

 - Example:  $Y = (\bar{A} \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot C)$



**SOP form does NOT directly lead to minimal logic**

# Canonical Sum of Products Form: Key Idea

---

- Any 1-bit function can be represented as a Sum of Products
- A “Product” is the Boolean AND that includes ALL input variables of the function → minterm
- The 1-bit Output of the Function can be represented as
  - Sum (OR) of all minterms that lead to a 1 in the Output
- Logically
  - The function evaluates to TRUE (i.e., output is 1) if ANY of the Products (minterms) causes the Output to be 1
  - SOP form represents the function as the SUM (OR) of all Products (minterms) that cause the Output to be 1

# Alternative Canonical Form: POS

## DeMorgan of SOP of $\bar{F}$

Find all the input combinations (maxterms) for which the output of the function is FALSE.

### Product of Sums (POS)

$$F = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)$$

product  
sums

Each sum term represents one of the "zeros" of the function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$F = \underbrace{(A + B + C)}_{\substack{0 \quad 0 \quad 0 \\ \text{This input}}}\underbrace{(A + B + \bar{C})}_{\substack{0 \quad 0 \quad 1 \\ \text{Activates this term}}}\underbrace{(A + \bar{B} + C)}_{\substack{0 \quad 1 \quad 0 \\ \text{This input}}}$$

For the given input, only the shaded sum term will equal 0


$$A + \bar{B} + C = 0 + \bar{1} + 0$$

Anything ANDed with 0 is 0; Output F will be 0

The function evaluates to FALSE (i.e., output is 0) if **any** of the Sums (maxterms) causes the output to be 0

# Consider $A=0, B=1, C=0$

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

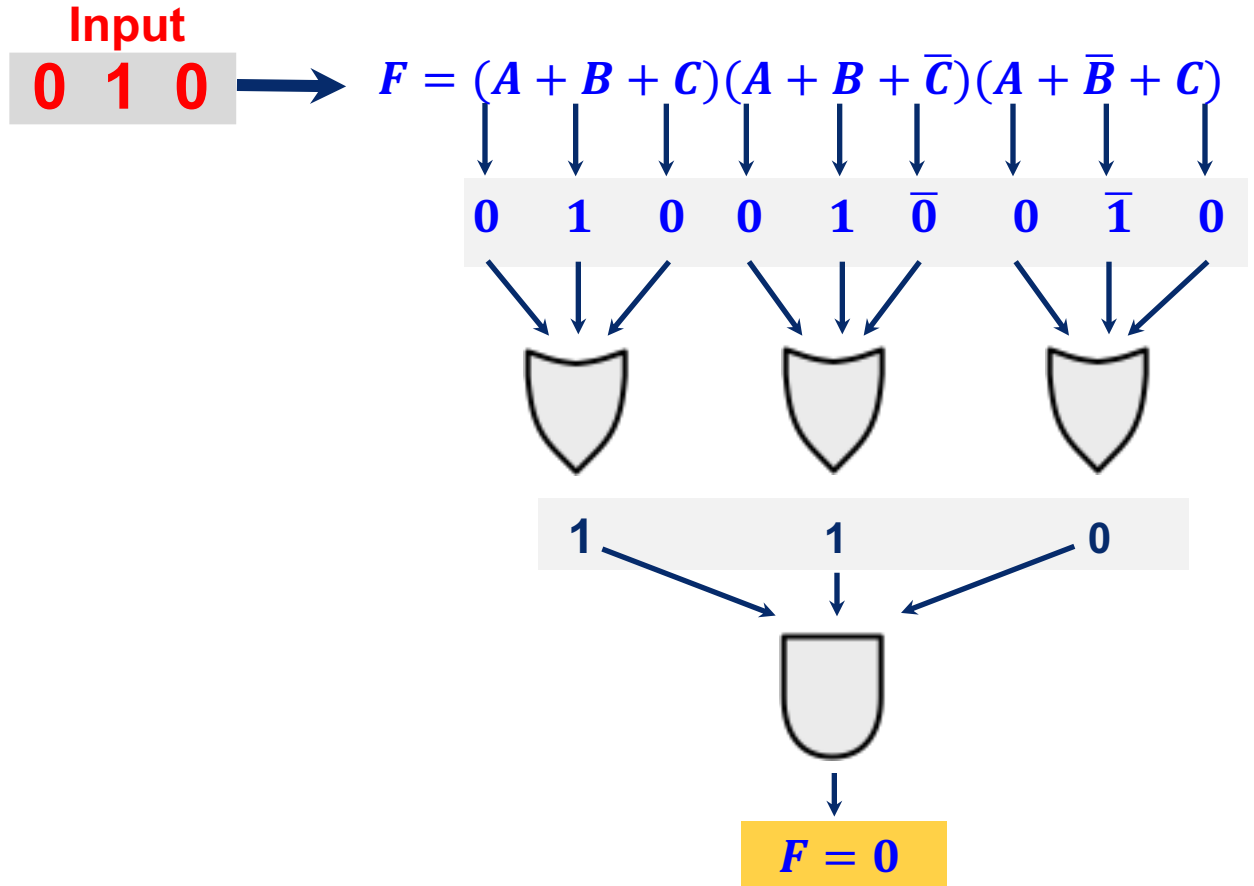

**Only one of the products will be 0, anything ANDed with 0 is 0**

**Therefore, the output is  $F = 0$**

# POS: How to Write It

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$F = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)$

$A \quad \bar{B} \quad C$   
 $A + \bar{B} + C$

## Maxterm form:

1. Find truth table rows where F is 0
2. 0 in input col → true literal
3. 1 in input col → complemented literal
4. OR the literals to get a Maxterm
5. AND together all the Maxterms

*Or just remember" POS of  $F$  is the same as the DeMorgan of SOP of  $\bar{F}$*

# Notation for the Canonical POS Form

## Product of Sums / Conjunctive Normal Form / Maxterm Expansion

$$F = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)$$

$$\prod M(0, 1, 2)$$

A	B	C	Maxterms
0	0	0	$A + B + C = M0$
0	0	1	$A + B + \bar{C} = M1$
0	1	0	$A + \bar{B} + C = M2$
0	1	1	$A + \bar{B} + \bar{C} = M3$
1	0	0	$\bar{A} + B + C = M4$
1	0	1	$\bar{A} + B + \bar{C} = M5$
1	1	0	$\bar{A} + \bar{B} + C = M6$
1	1	1	$\bar{A} + \bar{B} + \bar{C} = M7$

Maxterm shorthand notation for a function of three variables

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Note that you form the maxterms around the “zeros” of the function

This is **not** the complement of the function!



# Useful Conversions

---

1. **Minterm to Maxterm conversion:**

rewrite minterm shorthand using maxterm shorthand  
replace minterm indices with the indices not already used

$$\text{E.g., } F(A, B, C) = \sum m(3, 4, 5, 6, 7) = \prod M(0, 1, 2)$$

2. **Maxterm to Minterm conversion:**

rewrite maxterm shorthand using minterm shorthand  
replace maxterm indices with the indices not already used

$$\text{E.g., } F(A, B, C) = \prod M(0, 1, 2) = \sum m(3, 4, 5, 6, 7)$$

3. **Expansion of F to expansion of  $\bar{F}$ :**

$$\begin{array}{lcl} \text{E. g., } F(A, B, C) = \sum m(3, 4, 5, 6, 7) & \longrightarrow & \bar{F}(A, B, C) = \sum m(0, 1, 2) \\ & & = \prod M(3, 4, 5, 6, 7) \\ & \longrightarrow & = \prod M(0, 1, 2) \end{array}$$

4. **Minterm expansion of F to Maxterm expansion of  $\bar{F}$ :**

rewrite in Maxterm form, using the same indices as F

$$\begin{array}{lcl} \text{E. g., } F(A, B, C) = \sum m(3, 4, 5, 6, 7) & \longrightarrow & \bar{F}(A, B, C) = \prod M(3, 4, 5, 6, 7) \\ & \longrightarrow & = \sum m(0, 1, 2) \\ & & = \prod M(0, 1, 2) \end{array}$$


# Logic Simplification (or Minimization)

---

- Using Boolean Algebra, we can simplify the SOP or POS form of any function in a methodical way
- Starting with the canonical SOP or POS form enables convenience and automation
  - Truth table → SOP/POS form → Boolean Simplification Rules
- **Example (full 1-bit adder – more later):**

$$S = F(A, B, C_{in})$$

$$C_{out} = G(A, B, C_{in})$$

 


$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$

# Logic Simplification Example: SOP Form

- **SOP (sum-of-products) form of function Y**

 - Example:  $Y = (\bar{A} \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot C)$




**SOP form does NOT directly lead to minimal logic**

# Logic Simplification Example: Simplified

---

- **SOP (sum-of-products) form of function Y**

 - Example:  $Y = (\overline{B} \cdot \overline{C}) + (A \cdot \overline{B})$



# Let's Cover Some Basic Combinational Blocks

# Combinational Building Blocks used in Modern Computers

# Recall: Common Logic Gates

## Buffer



A	Z
0	0
1	1

## AND



A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

## OR



A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

## XOR



A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

## Inverter



A	Z
0	1
1	0

## NAND



A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

## NOR



A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

## XNOR



A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1

# Combinational Building Blocks

---

- Combinational logic is often grouped into larger building blocks to build more **complex systems**
  - Hides the **unnecessary gate-level details** to emphasize the function of the building block
  - We now examine:
    - Decoder
    - Multiplexer
    - Full adder
    - PLA (Programmable Logic Array)
-




# Decoder

# Decoder

---



- “Input pattern detector”
- $n$  inputs and  $2^n$  outputs
- Exactly one of the outputs is 1 and all the rest are 0s
- The **output** that is logically 1 is the output corresponding to the input **pattern** that the logic circuit is expected to detect
- Example: 2-to-4 decoder

$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

  
# Decoder (I)

- $n$  inputs and  $2^n$  outputs
- Exactly one of the outputs is 1, and all the rest are 0s
- The **output** that is logically 1 is the output corresponding to the input **pattern** that the logic circuit is expected to detect


 
# Decoder (II)

- The decoder is useful in determining how to interpret a bit pattern
  - **It could be the address of a location in memory, that the processor intends to read from**
  - **It could be an instruction in the program and the processor needs to decide what action to take (based on *instruction opcode*)**




# Multiplexer (MUX)

# Multiplexer (MUX), or Selector

---



- **Selects** one of the  $N$  inputs to connect it to the output
  - based on the value of a  $\log_2 N$ -bit control input called **select**
- Example: 2-to-1 MUX

$S$	$D_1$	$D_0$	$Y$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 
  
# Multiplexer (MUX), or Selector (II)


- **Selects** one of the  $N$  inputs to connect it to the output
  - based on the value of a  $\log_2 N$ -bit control input called **select**
- Example: 2-to-1 MUX



# Multiplexer (MUX), or Selector (III)

- The output C is always connected to either the input A or the input B
  - Output value depends on the value of the **select line S**



<b>S</b>	<b>C</b>
0	A
1	B

 

- **Your task:** Draw the schematic for an 4-input (4:1) MUX
  - Gate level: as a combination of basic AND, OR, NOT gates
  - Module level: As a combination of 2-input (2:1) MUXes




# A 4-to-1 Multiplexer

  

# Aside: Logic Using Multiplexers


- Multiplexers can be used as lookup tables to perform logic functions

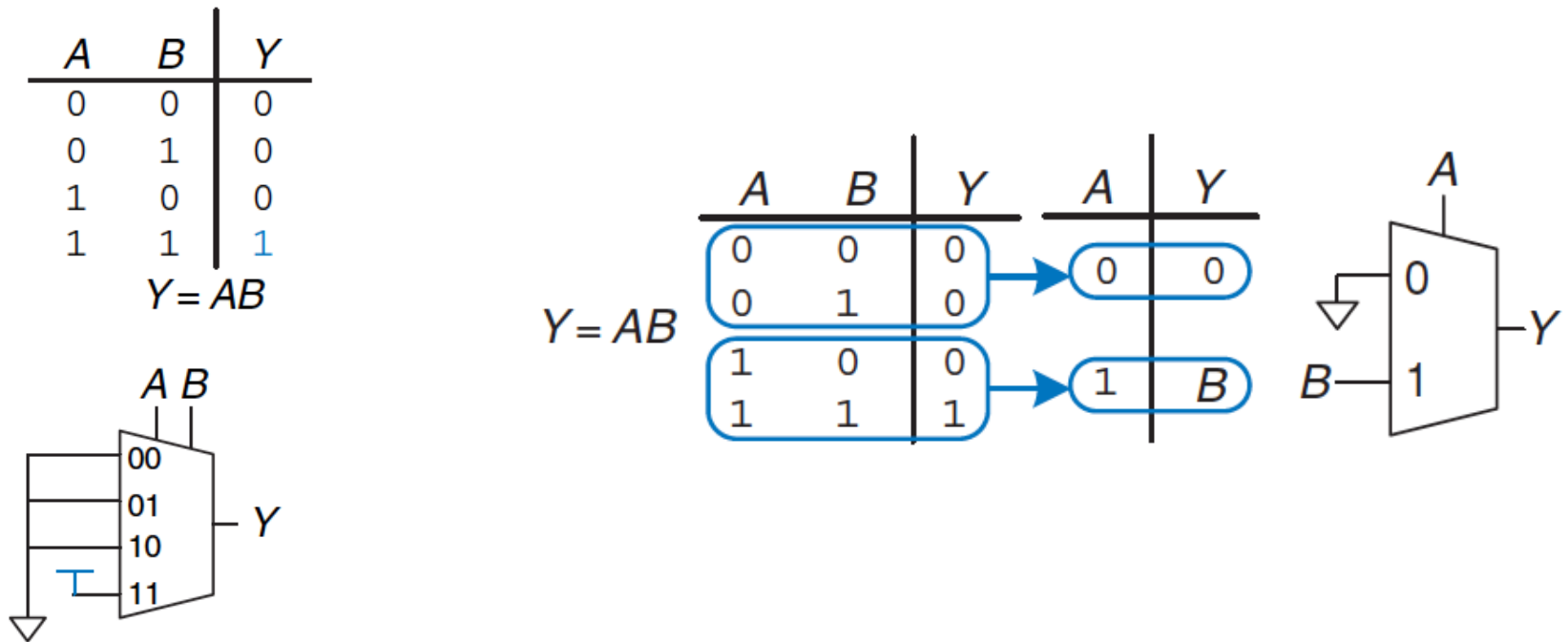

**Figure 2.59** 4:1 multiplexer implementation of two-input AND function
 
# Aside: Logic Using Multiplexers (II)

- Multiplexers can be used as lookup tables to perform logic functions




# Aside: Logic Using Multiplexers (III)

- Multiplexers can be used as lookup tables to perform logic functions


<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0
 
$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$



# 8-Input Lookup Table (LUT)

## ■ 3-bit input LUT (3-LUT)

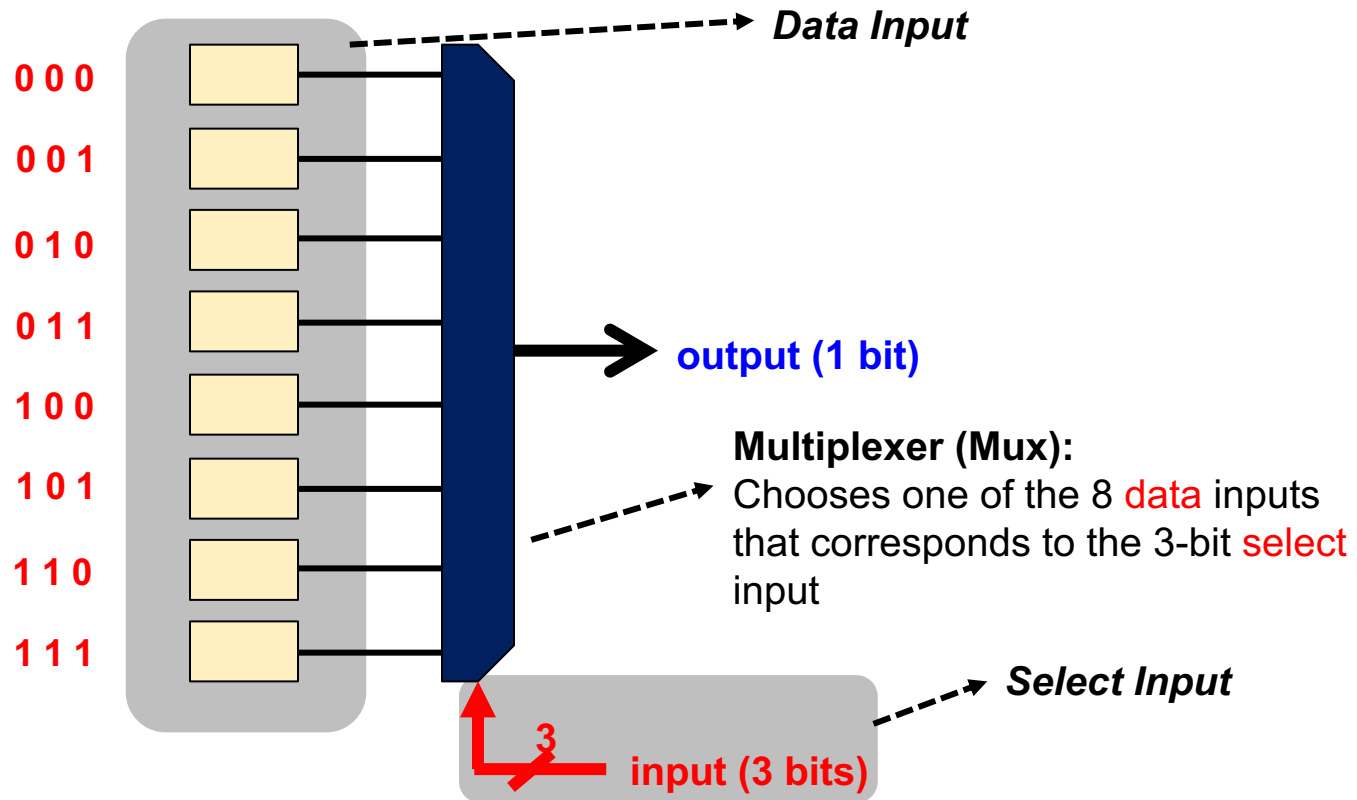

3-LUT can implement  
**any** 3-bit input function

# An Example of Programming a LUT

- Let's implement a function that outputs '1' when there are at least two '1's in a 3-bit input

In C:


```
int count = 0;
for(int i = 0; i < 3; i++) {
    count += input & 1;
    input = input >> 1;
}

if(count > 1) return 1;

return 0;
```


```
switch(input){
    case 0:
    case 1:
    case 2:
    case 4:
        return 0;
    default:
        return 1;}
```

In an FPGA:

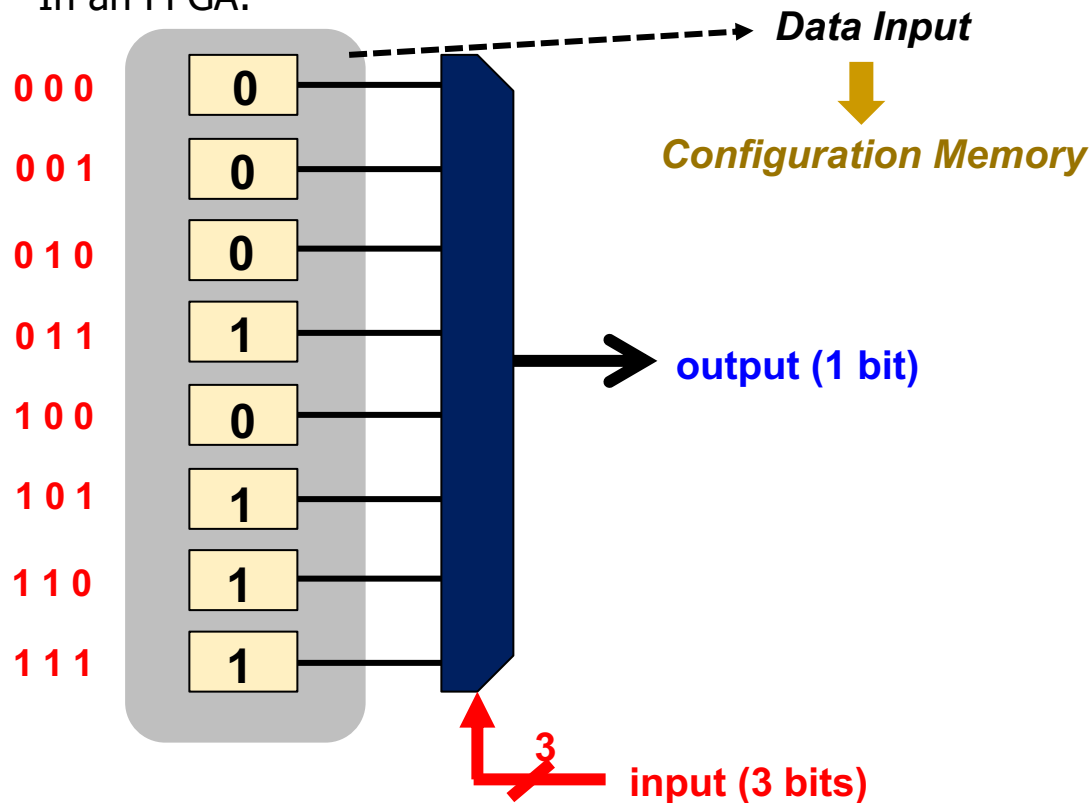

# Aside: Logic Using Decoders (I)

- Decoders can be combined with OR gates to build logic functions.

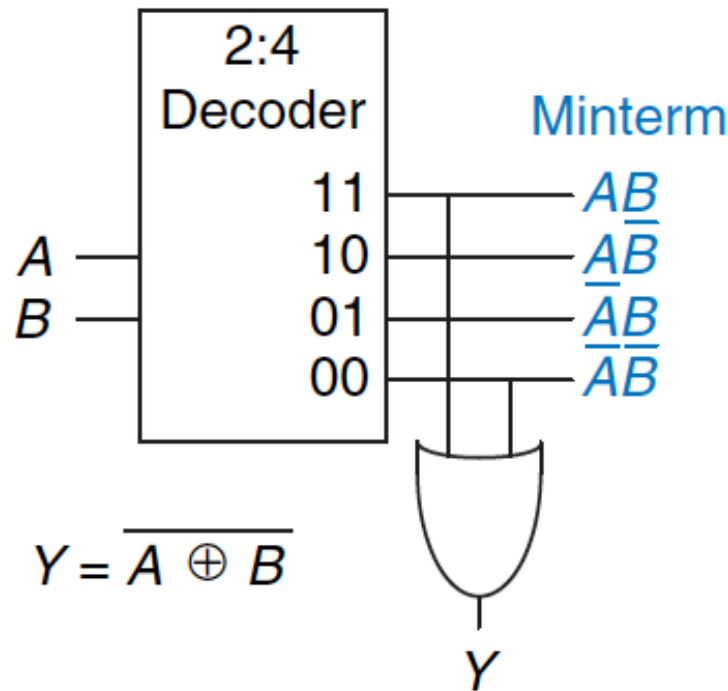

**Figure 2.65** Logic function using decoder


# Full Adder



# Full Adder (I)

## ■ Binary addition

- Similar to decimal addition
- From right to left
- One column at a time
- One sum and one carry bit

$$\begin{array}{r} a_{n-1}a_{n-2} \dots a_1a_0 \\ b_{n-1}b_{n-2} \dots b_1b_0 \\ C_n C_{n-1} \dots C_1 \\ \hline S_{n-1} \dots S_1S_0 \end{array}$$


 
- Truth table of binary addition on **one column** of bits within two n-bit operands

$a_i$	$b_i$	$carry_i$	$carry_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Full Adder (II)

## ■ Binary addition

- N 1-bit additions
- **SOP of 1-bit addition**




$$\begin{array}{r} a_{n-1}a_{n-2} \dots a_1a_0 \\ b_{n-1}b_{n-2} \dots b_1b_0 \\ \hline c_n c_{n-1} \dots c_1 \\ \hline S_{n-1} \dots S_1S_0 \end{array}$$

↓

$a_i$	$b_i$	$carry_i$	$carry_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

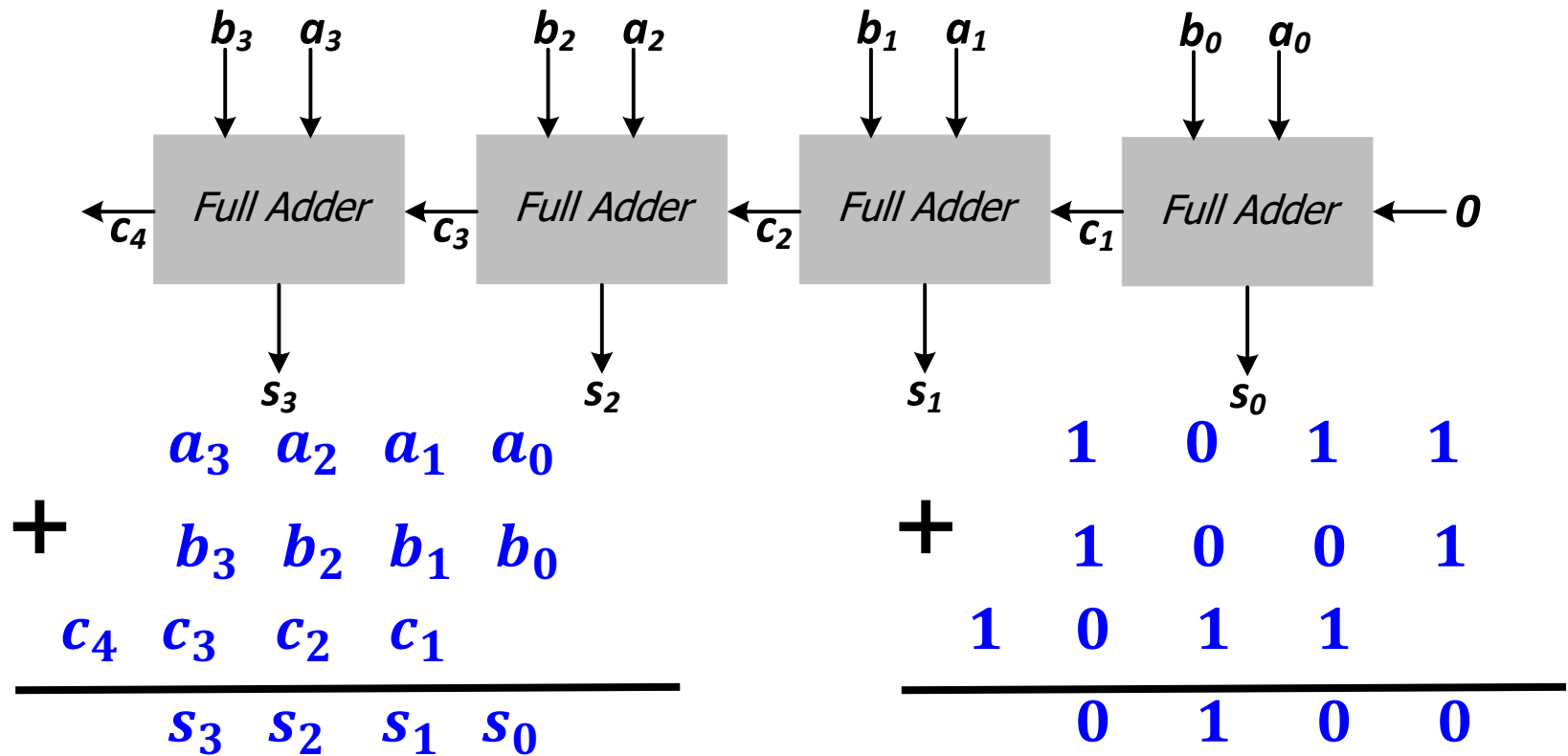
# 4-Bit Adder from Full Adders

- Creating a **4-bit adder** out of 1-bit full adders
  - To add two 4-bit binary numbers A and B




# Adder Design: Ripple Carry Adder

---

 


**Figure 5.5** 32-bit ripple-carry adder
 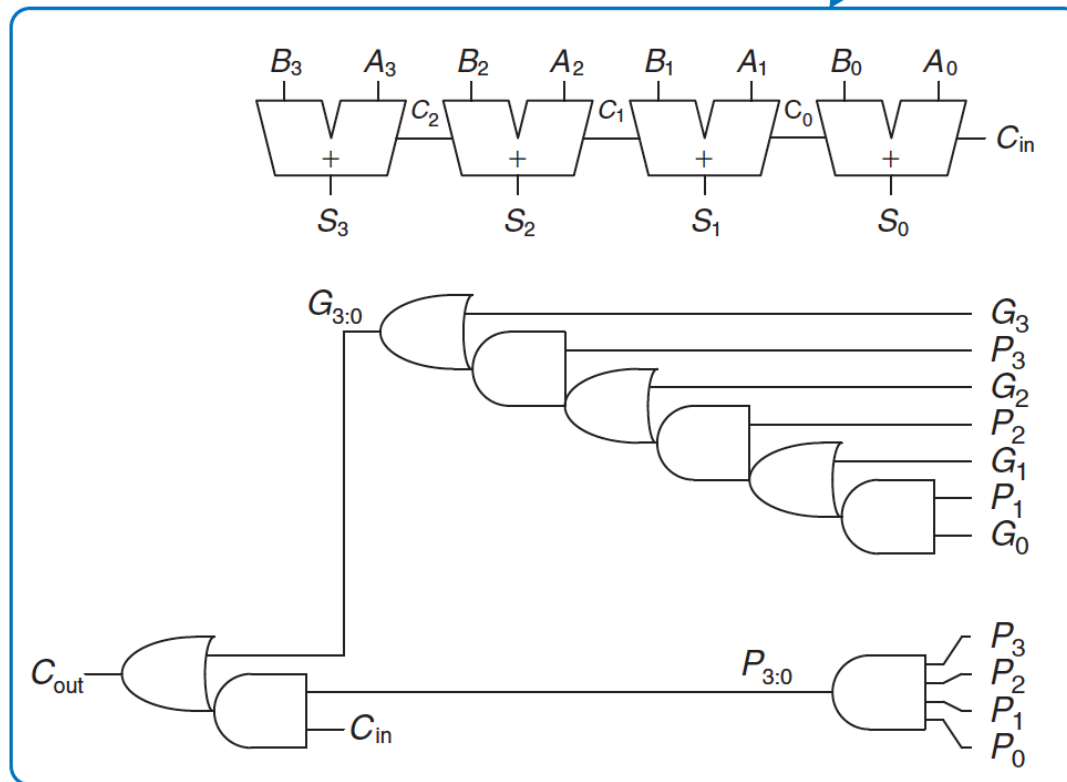
# Adder Design: Carry Lookahead Adder



(a)



(b)

**Example of  
logic specialization:  
Specialized logic for  
fast carry generation**


# Programmable Logic Array (PLA)

# PLA: Recall: SOP Form

---

- **SOP (sum-of-products) leads to two-level logic**

 - Example:  $Y = (\bar{A} \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot C)$



---

A PLA enables the two-level SOP implementation of **any** N-input M-output function

# The Programmable Logic Array (PLA)


- The below logic structure is a very **common** building block for implementing any collection of logic functions one wishes to

- An **array** of AND gates followed by an **array** of OR gates

- **How do we determine the number of AND gates?**

- **Remember SOP:** the number of possible minterms
- For an n-input logic function, we need a PLA with  $2^n$  n-input AND gates

 - **How do we determine the number of OR gates?** The number of output columns in the truth table




A PLA enables the two-level SOP implementation of **any** N-input M-output function


 
# The Programmable Logic Array (PLA)

- How do we implement a logic function?
  - Connect the output of an AND gate to the input of an OR gate if the corresponding minterm is included in the SOP
  - This is a simple programmable logic construct


■ **Programming a PLA:** we program the connections from AND gate outputs to OR gate inputs to implement a desired logic function




- Have you seen any other type of programmable logic?
  - Yes! An FPGA...
  - An FPGA uses more advanced structures, as we see in the labs

# PLA Example (I)


---

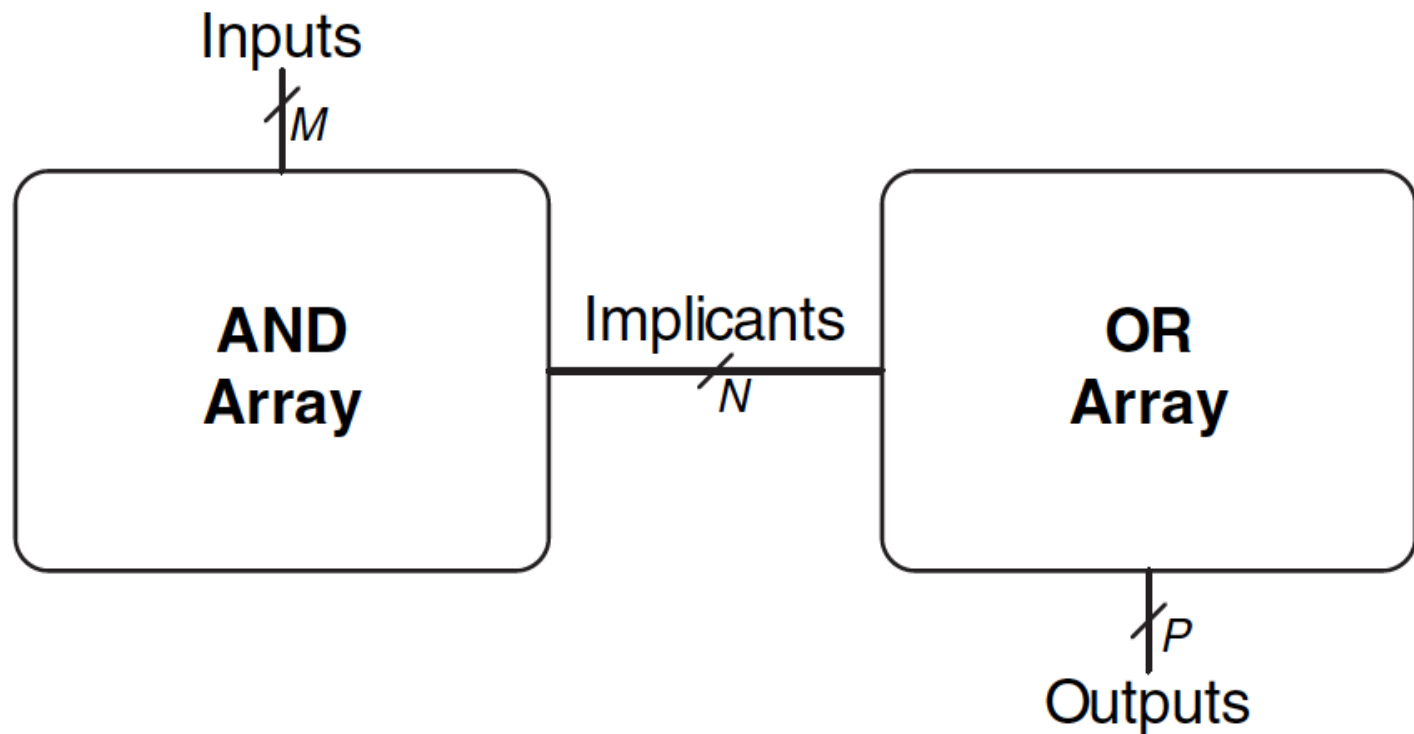


# PLA Example Function (II)

 

# PLA Example Function (III)

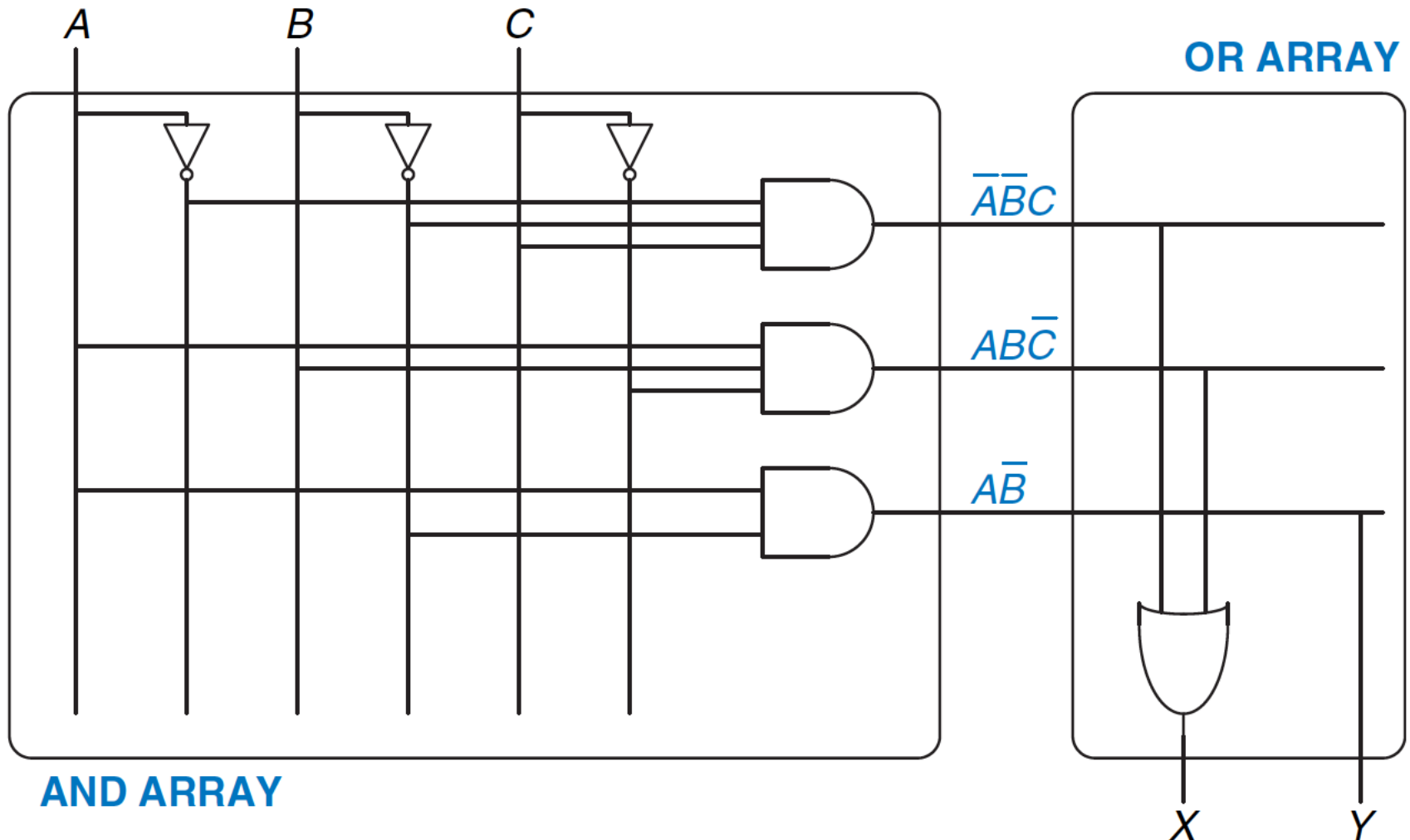

# Implementing a Full Adder Using a PLA

 


Truth table of a full adder

$a_i$	$b_i$	$carry_i$	$carry_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

This input should not be connected to any outputs

We do not need this output

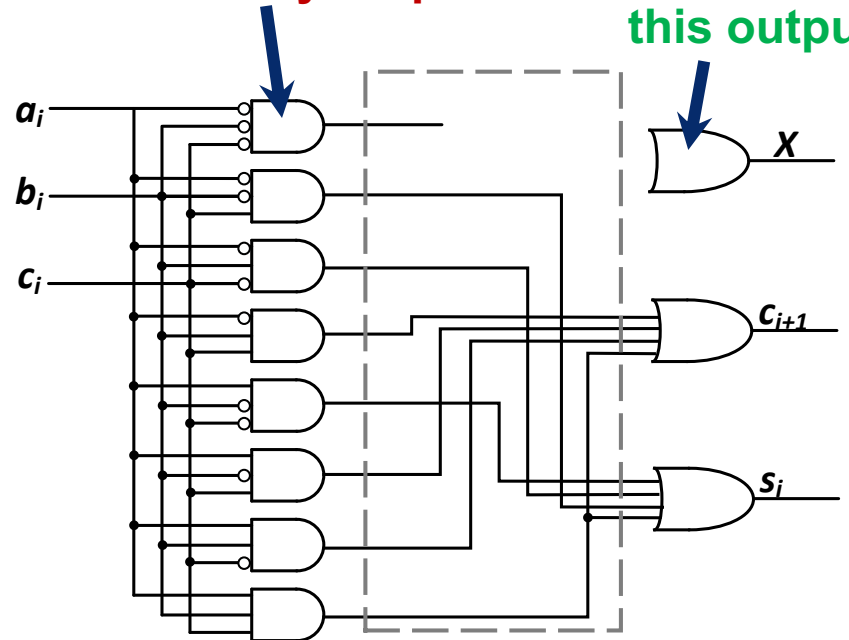

# Logical Completeness

# Logical (Functional) Completeness

---

- **Any logic function** we wish to implement could be accomplished with a PLA
  - PLA consists of **only** AND gates, OR gates, and inverters
  - We just have to program connections based on SOP of the intended logic function
- The set of gates {AND, OR, NOT} is **logically complete** because we can build a circuit to carry out the specification of **any truth table** we wish, without using any other kind of gate
- NAND is also logically complete. So is NOR.
  - **Your task:** Prove this.

# More Combinational Blocks



# More Combinational Building Blocks

---



- H&H Chapter 2 in full
  - Required Reading
  - E.g., see Tri-state Buffer and Z values in Section 2.6
- H&H Chapter 5
  - Will be required reading soon.
- You will benefit greatly by reading the “combinational” parts of Chapter 5 soon.
  - Sections 5.1 and 5.2

# Comparator
  
# Equality Checker (Compare if Equal)

---


- Checks if two N-input values are exactly the same
- Example: 4-bit Comparator



# ALU (Arithmetic Logic Unit)

# ALU (Arithmetic Logic Unit)

- Combines a variety of arithmetic and logical operations into a single unit (that performs only one function at a time)
- Usually denoted with this symbol:

 

**Figure 5.14** ALU symbol


**Table 5.1** ALU operations

$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND $\bar{B}$
101	A OR $\bar{B}$
110	A - B
111	SLT

# Example ALU (Arithmetic Logic Unit)

**Table 5.1 ALU operations**

$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND $\bar{B}$
101	A OR $\bar{B}$
110	A - B
111	SLT

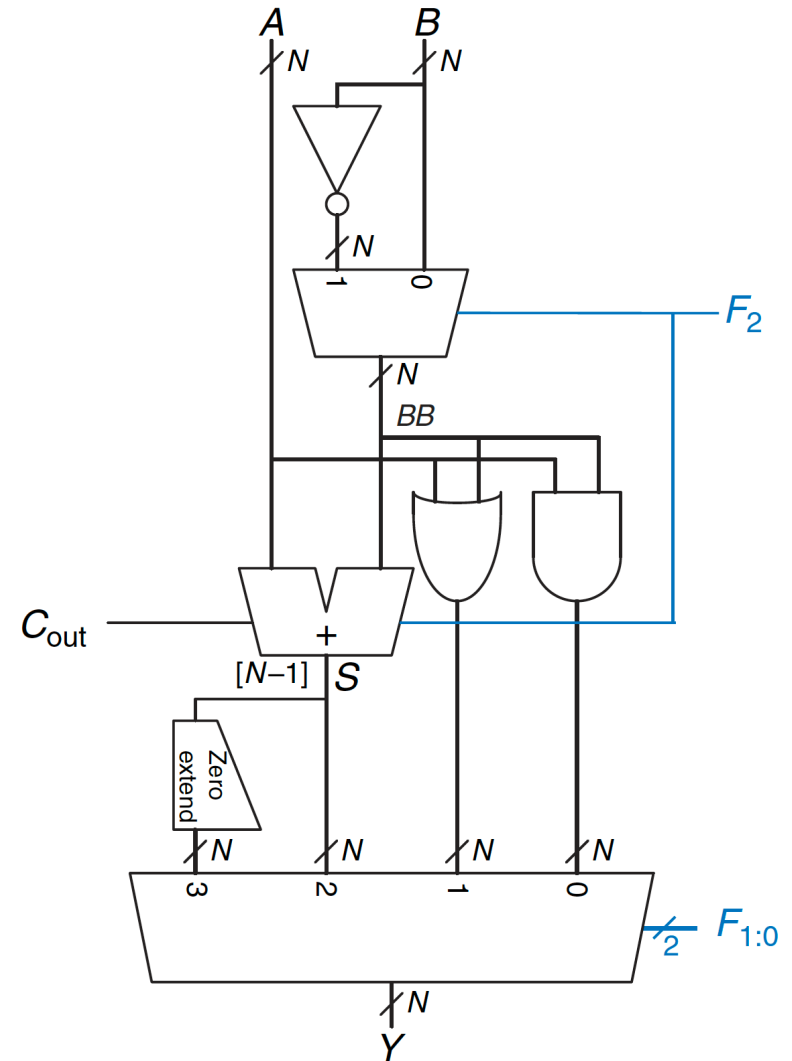

# More Combinational Building Blocks

---

- See H&H Chapter 5.2 for
  - Subtractor (using 2's Complement Representation)
  - Shifter and Rotator
  - Multiplier
  - Divider
  - ...

# More Combinational Building Blocks

---

- H&H Chapter 2 in full
  - Required Reading
  - E.g., see Tri-state Buffer and Z values in Section 2.6
- H&H Chapter 5
  - Will be required reading soon.
- You will benefit greatly by reading the “combinational” parts of Chapter 5 soon.
  - Sections 5.1 and 5.2




# Tri-State Buffer
 
# Tri-State Buffer

---

- A tri-state buffer enables gating of different signals onto a wire



**A tri-state buffer  
acts like a switch**

**Figure 2.40** Tristate buffer

- **Floating signal (Z):** Signal that is not driven by any circuit
  - Open circuit, floating wire


# Example: Use of Tri-State Buffers

---

- Imagine a wire connecting the CPU and memory
  - At any time only the CPU or the memory can place a value on the wire, both not both
  - You can have two tri-state buffers: one driven by CPU, the other memory; and ensure at most one is enabled at any time


# Example Design with Tri-State Buffers

---

 


# Another Example

---

 


# Multiplexer Using Tri-State Buffers

 



$$Y = D_0 \bar{S} + D_1 S$$

**Figure 2.56** Multiplexer using tri-state buffers

 

# Recall: A 4-to-1 Multiplexer

---

  

# We Covered Combinational Logic Blocks


---

- Basic logic gates (AND, OR, NOT, NAND, NOR, XOR)
  - Decoder
  - Multiplexer
  - Full Adder
  - Programmable Logic Array (PLA)
  - Comparator
  - Arithmetic Logic Unit (ALU)
  - Tri-State Buffer
- 
- Standard form representations: SOP & POS
  - Logical completeness
  - Logic simplification via Boolean Algebra



# Logic Simplification using Boolean Algebra Rules


# Recall: Full Adder in SOP Form Logic

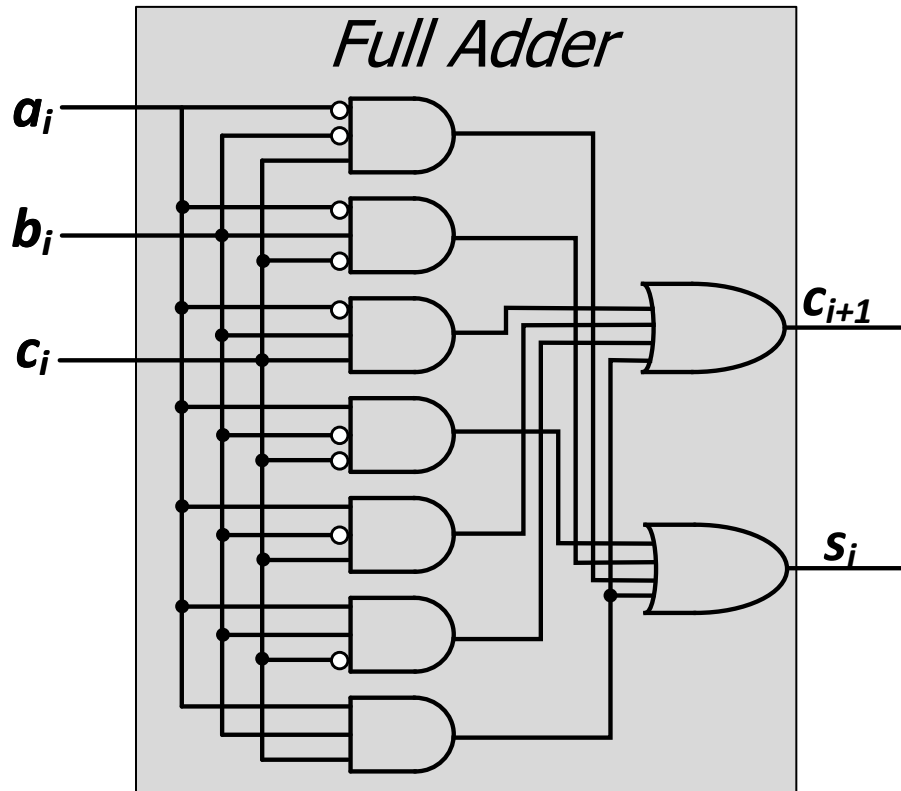

$a_i$	$b_i$	$carry_i$	$carry_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Goal: Simplified Full Adder

---

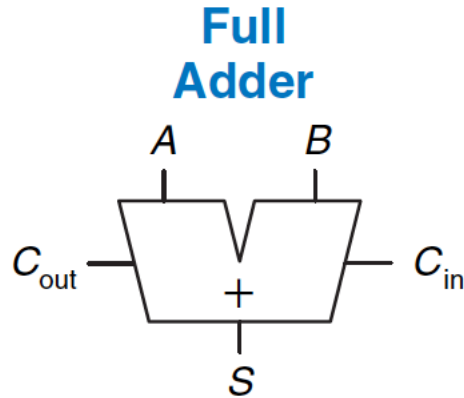

$$S = A \oplus B \oplus C_{in} \quad \text{3-input XOR}$$
$$C_{out} = AB + AC_{in} + BC_{in} \quad \text{3-input majority}$$

$C_{in}$	$A$	$B$	$C_{out}$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

**How do we simplify Boolean logic?**

**How do we automate simplification?**

# Quick Recap on Logic Simplification

---

- The original Boolean expression (i.e., logic circuit) may not be optimal

$$F = \sim A(A + B) + (B + AA)(A + \sim B)$$

- Can we reduce a given Boolean expression to an equivalent expression **with fewer terms?**

$$F = A + B$$

- The **goal** of logic simplification:
  - **Reduce** the number of gates/inputs
  - **Reduce** implementation cost (and potentially latency & power)  
**A basis for what the automated design tools are doing today**

# Logic Simplification

- Systematic techniques for simplifications

- amenable to automation

**Key Tool: The Uniting Theorem** —  $F = A\bar{B} + AB$

A	B	F
0	0	0
0	1	0
1	0	1
1	1	1

$$F = A\bar{B} + AB = A(\bar{B} + B) = A(1) = A$$

B's value changes within the rows where F=1 ("ON set")

A's value does NOT change within the ON-set rows

**If an input (B) can change without changing the output, that input value is not needed**

**→ B is eliminated, A remains**

A	B	G
0	0	1
0	1	0
1	0	1
1	1	0

$$G = \bar{A}\bar{B} + A\bar{B} = (\bar{A} + A)\bar{B} = \bar{B}$$

B's value stays the same within the ON-set rows

A's value changes within the ON-set rows

**→ A is eliminated, B remains**

# Logic Simplification

- Systematic techniques for simplifications

- amenable to automation

**Key Tool: The Uniting Theorem** —  $F = A\bar{B} + AB$

A	B	F
0	0	0
0	1	0
1	0	1
1	1	1

$$F = A\bar{B} + AB = A(\bar{B} + B) = A(1) = A$$

**Essence of Simplification:**

Find two-element subsets of the ON-set where only one variable changes its value. This single varying variable *can be eliminated!*

value is not needed

→ B is eliminated, A remains

A	B	G
0	0	1
0	1	0
1	0	1
1	1	0

$$G = \bar{A}\bar{B} + A\bar{B} = (\bar{A} + A)\bar{B} = \bar{B}$$

B's value stays the same within the ON-set rows


A's value changes within the ON-set rows

→ A is eliminated, B remains

# Logic Simplification Example: Priority Circuit
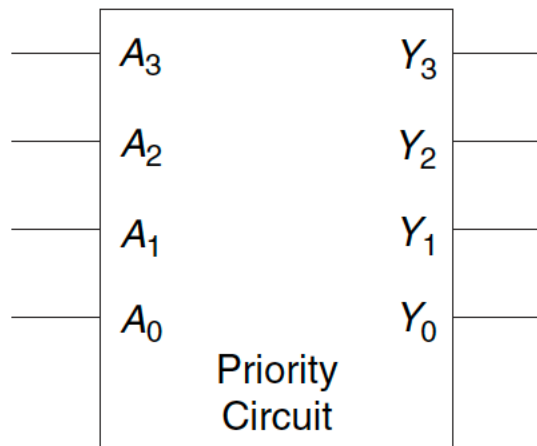
## ■ Priority Circuit

- Inputs: "Requestors" with priority levels
- Outputs: "Grant" signal for each requestor
- Example 4-bit priority circuit
- Real life example: Imagine a bus requested by 4 processors



$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0


# Simplified Priority Circuit

- Priority Circuit
  - Inputs: "Requestors" with priority levels
  - Outputs: "Grant" signal for each requestor
  - Example 4-bit priority circuit

$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

**Figure 2.29** Priority circuit truth table with don't cares (X's)

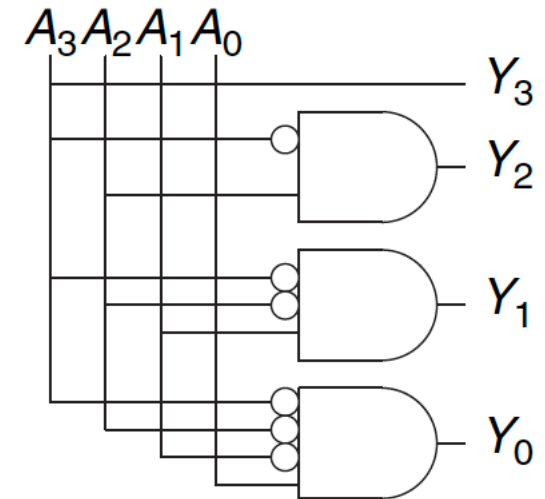

X (Don't Care) means *I don't care what the value of this input is*



# Logic Simplification: Karnaugh Maps (K-Maps)

# Karnaugh Maps are Fun...

---

- A pictorial way of minimizing circuits by visualizing opportunities for simplification
- They are for you to **study on your own...**
  
- See backup slides
- Read H&H Section 2.7

# We Are Done with Combinational Logic

---

- Building blocks of modern computers
    - Transistors
    - Logic gates
  - Combinational circuits
  - Boolean algebra
  - Using Boolean algebra to represent combinational circuits
  - Basic combinational logic blocks
  - Simplifying combinational logic circuits
-

# Backup Slides on Karnaugh Maps (K-Maps)

# Complex Cases

---

- One example

$$Cout = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

- Problem

- Easy to see how to apply Uniting Theorem...
- Hard to know if you applied it in all the right places...
- ...especially in a function of many more variables

- Question

- Is there an easier way to find potential simplifications?
- i.e., potential applications of Uniting Theorem...?

- Answer

- Need an intrinsically *geometric* representation for Boolean  $f( )$
- Something we can draw, see...

# Karnaugh Map

- Karnaugh Map (K-map) method
  - K-map is an alternative method of representing the **truth table** that helps **visualize adjacencies** in up to 6 dimensions
  - Physical adjacency  $\leftrightarrow$  Logical adjacency

**2-variable K-map**

<b>A</b> \ <b>B</b>	<b>0</b>	<b>1</b>
<b>0</b>	00	01
<b>1</b>	10	11

**3-variable K-map**

<b>BC</b> \ <b>A</b>	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>0</b>	000	001	011	010
<b>1</b>	100	101	111	110


**4-variable K-map**

<b>CD</b> \ <b>AB</b>	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>00</b>	0000	0001	0011	0010
<b>01</b>	0100	0101	0111	0110
<b>11</b>	1100	1101	1111	1110
<b>10</b>	1000	1001	1011	1010

**Numbering Scheme: 00, 01, 11, 10 is called a “Gray Code” — only a *single bit (variable) changes* from one code word and the next code word**

# Karnaugh Map Methods

<i>A</i> \ <i>BC</i>	00	01	11	10
0	000	001	011	010
1	100	101	111	110

 

**K-map adjacencies go "around the edges"**  
**Wrap around from first to last column**  
**Wrap around from top row to bottom row**

# K-map Cover - 4 Input Variables

CD \ AB	00	01	11	10
00	1	0	0	1
01	0	1	0	0
11	1	1	1	1
10	1	1	1	1

$$F(A, B, C, D) = \sum m(0, 2, 5, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$F = A + \bar{B}\bar{D} + B\bar{C}D$$

**Strategy for "circling" rectangles on Kmap:**

**Biggest "oops!" that people forget:**



# Logic Minimization Using K-Maps

---


- Very simple guideline:
  - Circle all the rectangular blocks of 1's in the map, using the fewest possible number of circles
    - Each circle should be as large as possible
  - Read off the implicants that were circled
  
- More formally:
  - A Boolean equation is minimized when it is written as a sum of the fewest number of prime implicants
  - Each circle on the K-map represents an implicant
  - The largest possible circles are prime implicants

# K-map Rules

---

- **What can be legally combined (circled) in the K-map?**
  - Rectangular groups of size  $2^k$  for any integer  $k$
  - Each cell has the same value (1, for now)
  - All values must be adjacent
    - Wrap-around edge is okay
- **How does a group become a term in an expression?**
  - Determine which literals are constant, and which vary across group
  - Eliminate varying literals, then AND the constant literals
    - constant 1 → use  $X$ , constant 0 → use  $\bar{X}$
- **What is a good solution?**
  - Biggest groupings → eliminate more variables (literals) in each term
  - Fewest groupings → fewer terms (gates) all together
  - OR together all AND terms you create from individual groups

# K-map Example: Two-bit Comparator

 


A	B	C	D	F1	F2	F3
0	0	0	0	1	0	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	0	1	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	1	0	0

## Design Approach:

Write a 4-Variable K-map  
for each of the 3  
output functions

# K-map Example: Two-bit Comparator (2)

**K-map for F1**

 


**F1 =**

A	B	C	D	F1	F2	F3
0	0	0	0	1	0	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	0	1	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	1	0	0

# K-map Example: Two-bit Comparator (3)

**K-map for F2**

 

**F2 =**

**F3 = ? (Exercise for you)**

A	B	C	D	F1	F2	F3
0	0	0	0	1	0	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	0	1	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	1	0	0

# K-maps with “Don’t Care”

- **Don’t Care** really means *I don’t care what my circuit outputs if this appears as input*
  - You have an engineering choice to use DON’T CARE patterns intelligently as 1 or 0 to better **simplify** the circuit

A	B	C	D	F	G
...					
0	1	1	0	X	X
0	1	1	1		
1	0	0	0	X	X
1	0	0	1		
...					

I can pick 00, 01, 10, 11  
independently of below

I can pick 00, 01, 10, 11  
independently of above

# Example: BCD Increment Function

- BCD (Binary Coded Decimal) digits
  - Encode decimal digits 0 - 9 with bit patterns  $0000_2$  —  $1001_2$
  - When **incremented**, the decimal sequence is 0, 1, ..., 8, 9, 0, 1

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

These input patterns **should never be encountered** in practice (hey -- it's a BCD number!)  
So, associated output values are **"Don't Cares"**

# K-map for BCD Increment Function

**A B**

**+**

**W X**

Z (without don't cares) =

Z (with don't cares) =

10	1		X	X
----	---	--	---	---

10			X	X
----	--	--	---	---

**Y**

	<b>CD</b>	00	01	11	10
<b>AB</b>	00		1		1
	01		1		1
	11	X	X	X	X
	10			X	X

**Z**

	<b>CD</b>	00	01	11	10
<b>AB</b>	00	1			1
	01	1			1
	11	X	X	X	X
	10	1		X	X

*A* *B* *C* *D*



# K-map Summary

---

- **Karnaugh maps** as a formal systematic approach for logic simplification
- 2-, 3-, 4-variable K-maps
- K-maps with “**Don't Care**” outputs
- H&H Section 2.7